

Total No. of Questions : 5 ] [ Total No. of Printed Pages : 4

Roll No. ....

**305(N)**

**B. E. (Third Semester) EXAMINATION, Dec., 2010**

**(New Scheme)**

**(Common for EC, EE, EI, EX & BM Engg. Branch)**

**NETWORK ANALYSIS**

*Time : Three Hours*

*Maximum Marks : 100*

*Minimum Pass Marks : 35*

**Note :** Attempt all questions. All questions carry equal marks.

1. (a) Discuss the properties of an ideal current source and an ideal voltage source. Explain how a voltage source can be converted into an equivalent current source and vice versa. 8
- (b) A  $5\mu\text{F}$  capacitor is connected in series with a coil having an inductance of  $50\text{ mH}$ . Determine the frequency of resonance, the resistance of coil, if a  $50\text{ V}$  source operating at resonance frequency causes a circuit current of  $10\text{ mA}$ . What is the  $Q$  factor of the coil ? 12

*Or*

- (a) Explain the terms 'tie-set matrix' and 'cut-set matrix' of a network with illustrative examples. 8
- (b) In the network shown in fig. 1 ahead, switch 'K' is closed at  $t = 0$ , connecting a source  $e^{-t}$  to the R-C network. At  $t = 0$ , it is observed that the capacitor voltage has the value  $v_c(0) = 0.5\text{ volt}$ . For the element values given, determine  $v_2(t)$ . 12

P. T. O.

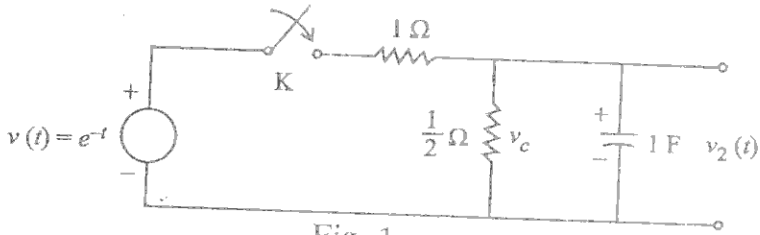


Fig. 1

2. (a) State and explain 'Maximum power transfer theorem' for an A. C. circuit. 6
- (b) For the network shown in fig. 2, replace the circuit to the left of terminals AB with a Thevenin's equivalent. Then determine the current in the  $2 - j2 \Omega$  impedance connected to the equivalent circuit. 14

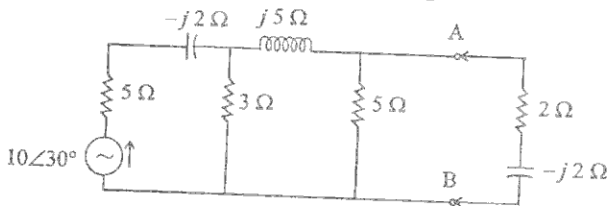


Fig. 2

Or

- (a) State and explain 'Millman's theorem'. 5
- (b) For the network shown in fig. 3, using Millman's theorem, find the current in the load impedance  $Z_L = (2 + j4) \Omega$ . 15

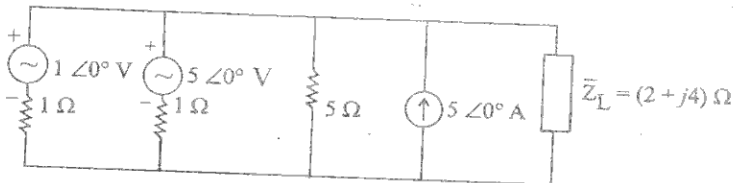


Fig. 3

3. (a) Show that the transform of any function delayed to begin at the time  $t = a$  is  $e^{-as}$  times the transform of the function when it begins at time  $t = 0$ . 6
- (b) The waveform shown in ahead fig. 4 is known as a staircase. Assuming that the staircase is not repeated,

write an equation for it in terms of unit-step functions. If this voltage is applied to an R-L series network with  $R = 1 \Omega$  and  $L = 1 \text{ H}$ , find the current  $i(t)$ . 14

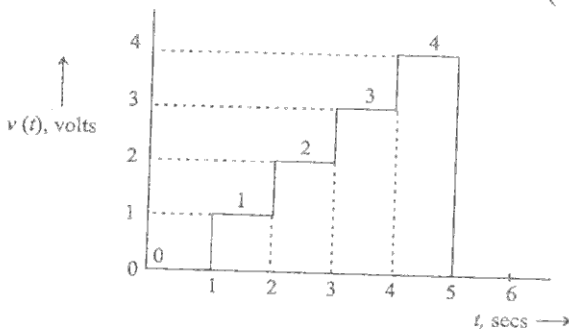


Fig. 4

Or

In the network shown in fig. 5, the switch K is thrown from position 1 to 2 at time  $t = 0$ . Just before the switch is thrown, the initial conditions are  $i_L(0_-) = 4 \text{ amp}$ ,  $v_C(0_-) = 4 \text{ volts}$ . Find the current  $i(t)$  after the switching action, using Laplace transformation method. 20

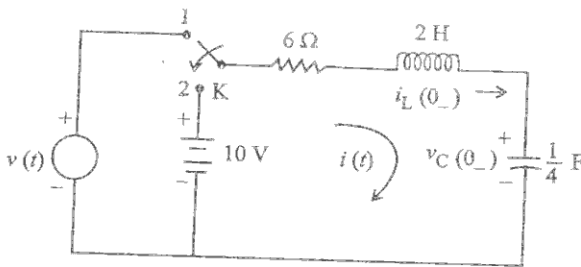


Fig. 5

4. (a) Discuss the effect of symmetry for a periodic function to determine the trigonometric Fourier series representation. 5
- (b) Find the trigonometric Fourier series for a half-wave rectified sine wave shown in fig. 6. 15

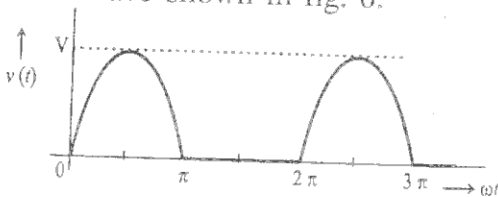


Fig. 6

Or

- (a) Explain the terms, 'even-symmetry' 'odd-symmetry' for periodic waveforms with Fourier series representation. 6
- (b) Find the trigonometric Fourier series for the waveform shown in fig. 7 and sketch the spectrum. 14

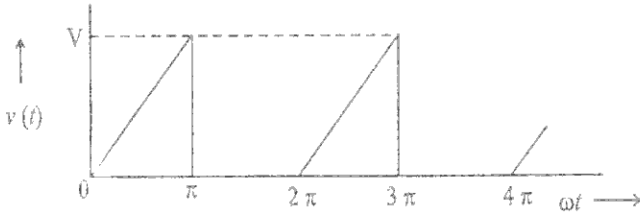


Fig. 7

5. (a) Define the terms, 'Driving point impedance' and 'Voltage ratio transfer function' with reference to two-port networks. 6
- (b) The network shown in fig. 8 contains resistors and controlled sources. For this network determine

$$G_{12}(s) = \frac{V_2(s)}{V_1(s)}$$

14

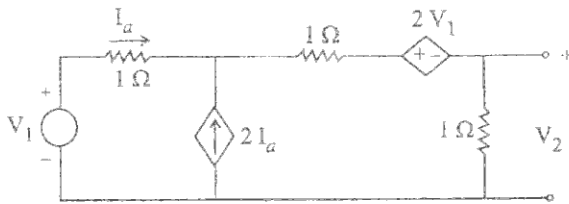


Fig. 8

Or

The network shown in fig. 9 is a bridged T, RC network. For the values given, find 'Y' and 'Z' parameters. 20

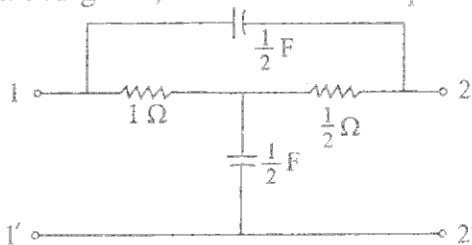


Fig. 9