

Roll No.

BM/CS/EI-303(N)

B. E. (Third Semester) EXAMINATION, June, 2010

(New Scheme)

(Common for BM, CS & EI Engg. Branch)

DIGITAL CIRCUITS AND SYSTEMS

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt any *five* questions. All questions carry equal marks.

1. (a) Convert the following :

(i) $(B65F)_{16} = ()_{10}$

(ii) $(153.25)_{10} = ()_2$

(iii) $(10110001101011)_2 = ()_8$

(iv) $(153)_{10} = ()_8$

(b) State and prove De Morgan's theorem.

2. (a) Simplify the following Boolean function with K-map :

$$F(W, X, Y, Z) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

(b) Simplify the following using Quine and McCluskey's method :

$$F(W, X, Y, Z) = \Sigma (0, 1, 2, 8, 10, 11, 14, 15)$$

P. T. O.

3. (a) Design a full adder with the help of truth table.
rgpvonline.com Explain the working of full adder by giving expressions for sum and carry in full adder.
- (b) Design a full subtractor using two half subtractor and an OR gate.
4. (a) Design a BCD adder and also give the rules of BCD addition.
- (b) Explain the working of Look-ahead carry generator.
5. (a) Explain the working of monostable multivibrators with the help of waveforms and circuit diagram.
- (b) Give a comparison of the following logic families : DTL, RTL and TTL.
6. (a) Design a 3 to 8 line decoder.
- (b) Explain the working of multiplexer and draw the detailed circuit of 4 to 1 line multiplexer.
7. (a) Design a 4 bit up-down binary counter.
- (b) Draw the circuit diagram of analog to digital converter and explain its working.
8. Write short notes on any *two* of the following :
- (i) Sample and hold circuit
 - (ii) V-F converter
 - (iii) Shift register
 - (iv) Code converter
 - (v) Schmitt trigger circuit