

[4]

5. a) What do you mean by a solid-state relay?
b) Explain why a zero-cross detector is required in motor control circuits.
c) Describe single-phase half-wave converter feeding a separately-excited dc motor.
d) Describe ignitron contractor, heat control circuit and weld timer electronic control in resistance welding.

OR

Discuss the application of power semiconductor devices to :

- i) Induction heating
ii) Dielectric heating.

Total No. of Questions :5]

[Total No. of Printed Pages :4

Roll No

EI/IC-504

B.E. V Semester

Examination, December 2016

Power Electronics

Time : Three Hours

Maximum Marks : 70

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
ii) All parts of each questions are to be attempted at one place.
iii) All questions carry equal marks, out of which part A and B (Max.50 words) carry 2 marks, part C (Max.100 words) carry 3 marks, part D (Max.400 words) carry 7 marks.
iv) Except numericals, Derivation, Design and Drawing etc.

1. a) List the semiconductor devices which can withstand :
i) Unipolar voltages
ii) Bipolar voltages
iii) Unidirectional current capability
b) Explain the switching performance of power transistor with relevant wave forms. Indicate clearly turn-on and turn-off times and their components.
c) What is IGBT? Give its basic structural features and working.
d) Describe various methods of triggering of the thyristor.

[2]

OR

Discuss the static and switching characteristics of IGBT and MOSFET.

2. a) Describe the principle of phase control.
- b) A single phase 230V, 1kW heater is connected across 1-phase, 230V, 50Hz supply through an SCR. Calculate the power absorbed in the heater element for firing angle delay of 90° .
- c) A single-phase one pulse SCR controlled converter feeds on RL load with a free-wheeling diode across the load. Discuss how free wheeling diode comes into play when supply voltage is passing through zero and becoming negative.
- d) A single-phase full converter charges a battery which offers a constant value of E . A resistor R is inserted to limit the battery charging current. Derive an expression for the average charging current in terms of V_m , E , R etc. On the assumption that each pair of SCRs is fired continuously in each half cycle. Take V_r as the voltage drop in conducting SCRs.

OR

A single phase full converter is supplied from 230V, 50Hz source. The load consists of $R = 10\Omega$ and a large inductance so as to render the load current constant. For a firing angle delay of 30° , determine :

- Average output voltage
- Average output current
- The power factor.

[3]

3. a) What are line commutated inverters? How do they operate?
- b) What is the purpose of connecting diodes in antiparallel with thyristors in inverter circuits?
- c) Describe the principle of dc chopper operation. Derive an expression for its average dc output voltage.
- d) Discuss the principle of working of a three-phase bridge inverter with an appropriate circuit diagram. Draw phase and line voltage wave forms on the assumption that each thyristor conducts of 120° and the resistive load is star connected.

OR

Describe a voltage commutated chopper with relevant current and voltage waveforms as a function of time.

4. a) What is an ac Voltage controller? List some of its industrial applications.
- b) Describe the operating principle of single-phase to single-phase step-up cycloconverter.
- c) Compare the merits of controlling the heater power by a triac using integral cycle control over the phase-angle control.
- d) Draw and explain the working of a single-phase a.c. voltage regulator feeding an inductive load.

OR

Describe the basic principle of working of single-phase to single phase step-down cycloconverter for both continuous and discontinuous conductions for a bridge type cycloconverter.