

Total No. of Questions : 8]

[Total No. of Printed Pages : 2

Roll No

CS-3003 (CBGS)**B.E., III Semester**

Examination, December 2017

Choice Based Grading System (CBGS)**Digital Circuit and Design**

Time : Three Hours

Maximum Marks : 70

- Note: i) Attempt any five questions.
ii) All questions carry equal marks.

1. a) Convert $(412)_{10}$ to
 - i) Binary
 - ii) Octal
 - iii) Hexadecimal
- b) What is universal gate? Implement AND, OR and NOT gates using NAND gates and OR gates.
2. a) Simplify the Boolean function using k map.
 $F(ABCD) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
- b) What is Boolean algebra write any three theorems of Boolean algebra?
3. a) Design and draw a full adder circuits.
- b) Explain monostable multibrater and write its application.
4. a) Compare RTL, DTL and TTL logic families.
- b) Draw and explain 4×1 multiplexer.

CS-3003 (CBGS)

160

PTO

[2]

5. a) What is counters? Differentiate Synchronous and Asynchronous counters.
- b) What is shift registers? Explain.
6. a) Implement a full adder circuit with a (3 to 8 lines) decoder and two OR gates.
- b) Why Analog to Digital converters is needed? Explain any one Digital converters.
7. a) Give a brief introduction of a semiconductor memories.
- b) What is a flip-flops? Explain with a suitable example.
8. Write a short notes (any three)
 - a) Schmitt trigger circuits
 - b) BCD adders
 - c) CMOS logic family
 - d) Half adder

161

CS-3003 (CBGS)