

Roll No

EE/EX/EI/BM - 305**B.E. III Semester**

Examination, December 2012

Network Analysis*Time : Three Hours**Maximum Marks : 70/100*

Note : 1. Answer Five questions, selecting One question from each unit.

2. All questions carry equal marks.

Unit - I

1. a) Explain clearly with the help of examples, 'tie-set' and 'cut-set' matrix of a network.
- b) Explain the concept of duality with the help of suitable example.
- c) Discuss the properties of series-resonant circuit.

OR

2. a) Discuss the initial conditions in a network. Briefly outline the procedure for evaluating the initial conditions in network problems.
- b) In the network shown in Fig. 1, the switch 'k' is changed from position 'a' to 'b' at $t = 0$. Find the values of i , $\frac{di}{dt}$

and $\frac{d^2i}{dt^2}$ at $t = 0+$.

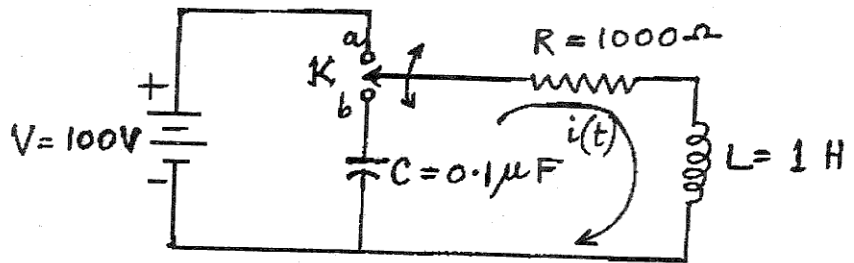


Figure-1

Unit - II

3. a) State and explain, 'Maximum power transfer theorem' for A.C. networks.
- b) In the network shown in Fig. 2, using Thevenin's theorem, find \bar{v}_2 , such that the current through the $(2 + j3)$ ohms impedance is zero.

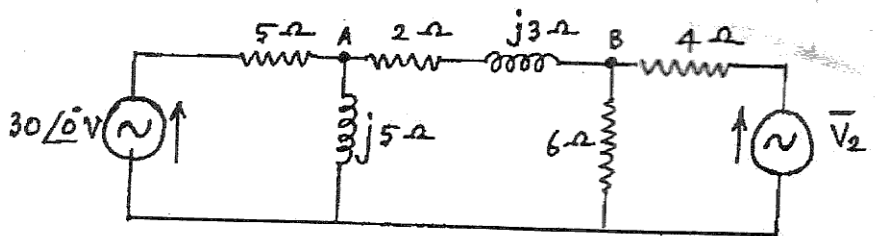


Figure-2

OR

4. a) State and explain the following:
- Millman's theorem
 - Reciprocity theorem
- b) In the network shown in Fig. 3, find the current flowing through 5Ω resistor (I), by superposition theorem.

[3]

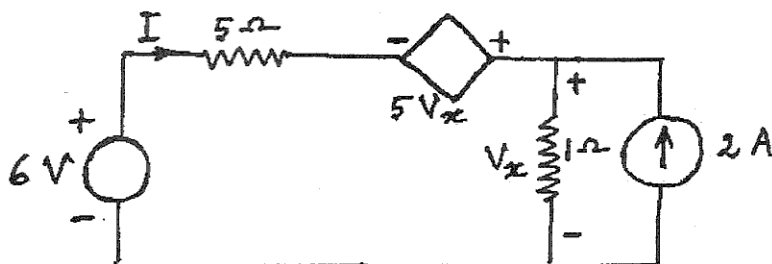


Figure-3

Unit - III

5. a) The waveform shown in Fig. 4, is non-recurring. Write an equation for $v(t)$ in terms of steps and related functions as needed. Find $v(s)$ for $v(t)$.

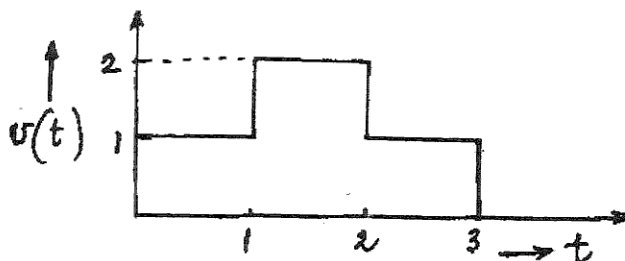


Figure-4

- b) Find the current $i(t)$ in a series R-L-C network as shown in Fig. 5, comprising $R = 5\ \Omega$, $L = 1\text{H}$ and $C = 0.25\text{F}$, when an impulse voltage $3\delta(t-1)$ is applied.

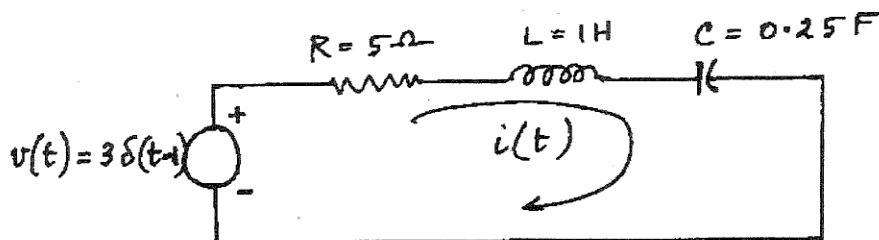


Figure-5

OR

6. a) Given the function, $F(s) = \frac{5(s+3)}{s(s+1)}$ find the initial value $f(0+)$ and the final value $f(\infty)$, without finding the inverse laplace transform of $F(s)$.
- b) If the capacitor is uncharged and the inductor current zero at $t = 0-$, in the network shown in Fig. 6, find $I(s)$, the transform of the current $i(t)$.

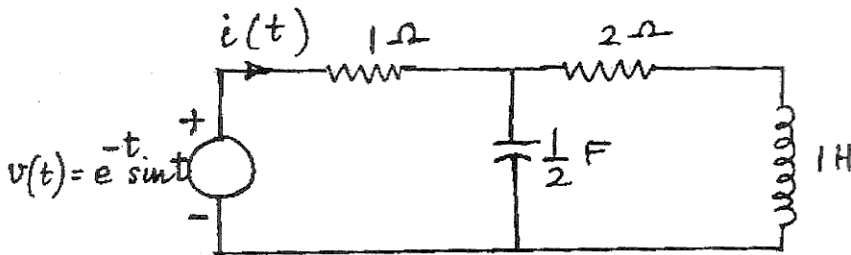


Figure-6

Unit - IV

7. a) Discuss the restrictions on poles and zeros locations in s-plane for driving point functions.
- b) Find the open circuit transfer impedance $\frac{V_2(s)}{I_1(s)}$ and open-circuit voltage ratio $\frac{V_2(s)}{V_1(s)}$ for the network shown in Fig. 7.

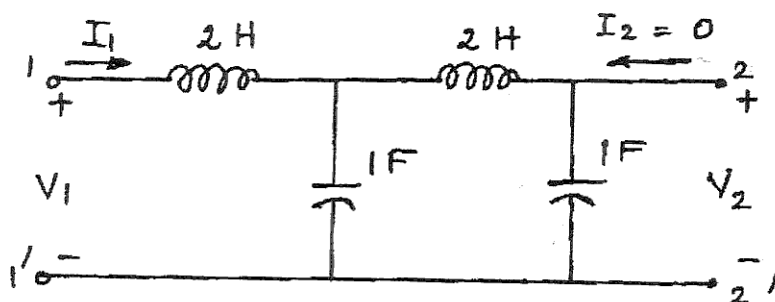


Figure-7

OR

8. Define open-circuit impedance (z) parameters of a two-port network. Determine ' z ' parameters for the network shown in Fig. 8.

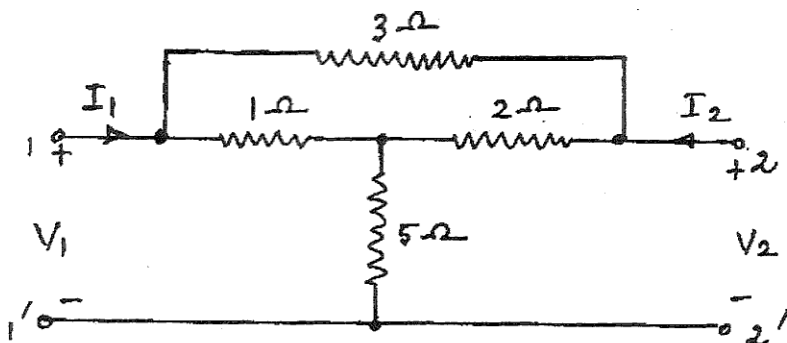


Figure-8

Unit - V

9. a) Discuss the effect of symmetry for a periodic function to determine the trigonometric Fourier series coefficients.
- b) Find the trigonometric Fourier series for the wave form shown in Fig. 9, and plot the line spectrum.

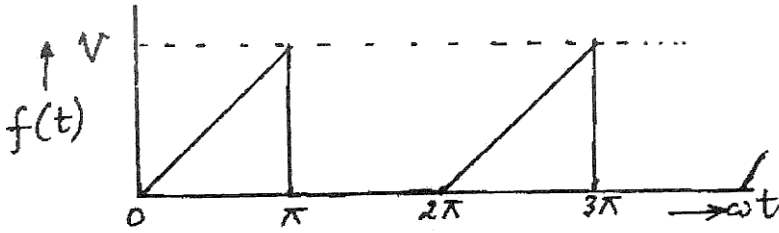


Figure-9

OR

10. a) Explain the terms 'Even symmetry' and 'odd symmetry' for periodic waveforms with Fourier series representation.
- b) Find the trigonometric Fourier series for the square wave shown in Fig. 10, and plot the line spectrum.

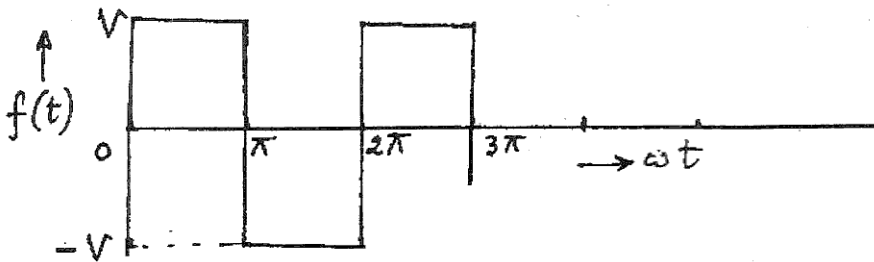


Figure-10
