

Total No. of Questions : 8]

[Total No. of Printed Pages : 2

Roll No .....

**IT-3003 (CBGS)****B.E. III Semester**

Examination, December 2017

**Choice Based Grading System (CBGS)****Digital Circuit and System****Time : Three Hours****Maximum Marks : 70****Note:** i) Attempt any five questions.

ii) All questions carry equal marks.

1. a) Convert the following numbers
  - i) Octal (25) into binary and Hexadecimal
  - ii) Hexadecimal (F4) into binary and octal
- b) Write DeMorgan's theorem and explain by taking a suitable example.
2. a)  $F = AB + CD + E$  implement this function with NOR gates.
- b) Explain multiplexer and demultiplexer circuits.
3. Simplify the Boolean function using k map.  
 $F(A, B, C, D) = \text{sum of } (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
4. a) Implement AND, OR, NOT or XOR gate with universal gates NOR and NAND.
- b) Explain the working of Decoder and Encoder.
5. Explain flip-flops. List the various types of flip-flops? Explain any two flip-flop with taking a suitable example.

IT-3003 (CBGS)

175

PTO

[2]

6. a) What do you understand by Bipolar and Unipolar logic families?
- b) Explain NMOS and CMOS logic.
7. a) Explain Schmitt trigger circuits.
- b) Write the purpose of analog to digital converters. Write any four application where analog to digital converter used.
8. Write a short notes (any two)
  - a) Astable multivibrator
  - b) RTL
  - c) Synchronous counters

\*\*\*\*\*

IT-3003 (CBGS)

176