

EX-403**B.E. IV Semester**

Examination, June 2013

Digital Electronics Logic Design-I**Time : Three Hours****Maximum Marks : 70/100**

- Note:** i) Attempt any one question from each unit.
 ii) Assume any missing data, if any.

rgpvonline.com**Unit - I**

1. a) Convert $(0.23)_8$ to Decimal and $(49.21)_{10}$ to octal.
 b) Convert $(152)_{10}$ to Hexadecimal and A43H to decimal.
 c) Add the following numbers
 $AB6 + B94$
 $11011 + 101011$

OR

2. a) Prove the following using De Morgan's law:

$$(A+B)(C+D) = \overline{\overline{A+B} + \overline{C+D}}$$
 Realize the above equation using only NOR gates.
 b) Simplify the Boolean function and realize.

$$A\overline{B}\overline{C} + \overline{A}BC + \overline{A}\overline{B}C$$

Unit - II

3. Simplify the following expression into sum of products using k-map.

$$F(A, B, C, D) = \sum(1, 3, 4, 5, 6, 7, 9, 12, 13).$$

OR

4. Construct a 5-to-32 line decoder using four 3-to-8 line decoders with enable and one 2-to-4 line decoder.

Unit - III

5. a) What do you mean by race condition of a flip-flop? How it can be avoided?
 b) Write steps involved in designing a sequential circuit.

OR

6. a) Explain the working of T-flip-flop with its timing diagram.
 b) Explain any one application of master slave flip-flop.

Unit - IV

7. Design a three-stage MOD-8 synchronous counter using T-flip-flops.

OR

8. What is a shift register? How a word is stored in a serial shift register.

Unit - V

9. a) Draw & explain the dual slope A to D converter.
 b) Explain ROM and its working. How is it different from PLA?

OR

10. Write short notes on any two of the following:
 a) Combinational PLDs
 b) D to A converter
 c) RAM.

rgpvonline.com
