

Total No. of Questions : 10] [Total No. of Printed Pages : 4

Roll No.

EC-802

B. E. (Eighth Semester) EXAMINATION, June, 2012

(Electronics & Communication Engg. Branch)

CMOS CIRCUIT DESIGN

(EC-802)

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt one question from each Unit. All questions carry equal marks.

Unit-I

1. (a) Discuss the small signal equivalent model for source follower. Derive equation for voltage gain of the source follower circuit. 10
- (b) Calculate the V_{out} of source follower circuit as shown in the following figure with :
 $(W/L)_{M_1} = 20/0.5$, $I_1 = 200 \mu A$, $V_{THO} = 0.6 V$,
 $2\phi F = 0.7 v$, $\mu_n \cos = 50 \mu A/v^2$ and $\gamma = 0.4 v^2$ and
 $V_{in} = 1.2 v$. 10

 


Fig. 1

P. T. O.

Or

2. (a) Discuss the high frequency model of a cascode stage. 10
 (b) Explain the effect of high frequency supply noise in differential pair. 10

Unit-II

3. The circuit shown in the following figure uses a resistor rather than a current source to define a tail current of 1 mA.

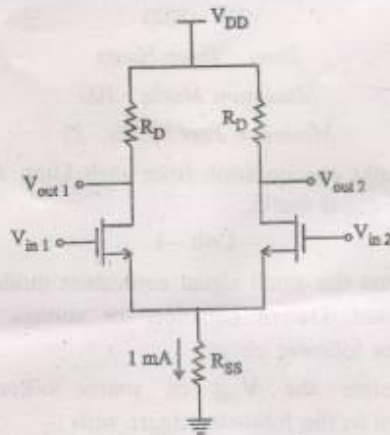


Fig. 2

Assume $(W/L)_{M_1 M_2} = 25/0.5$, $\mu_n \cos = 50 \mu \text{ A}/\text{V}^2$,
 $V_{TH} = 0.6 \text{ V}$, $\lambda = \gamma = 0$ and $V_{DD} = 3 \text{ V}$: 20

- (a) What is the required input common mode for which R_{SS} sustain 0.5 V ?
 (b) Calculate R_D for a differential gain of 5.
 (c) What happens at the output if the input common mode level is 50 mV higher than the part (a) of this problem ?

Or

4. (a) Explain in brief the different properties of feedback circuit. 10
(b) Explain the voltage to voltage type of feedback topologies. 10

Unit - III

5. Explain why a single common source stage does not oscillate if it is placed in a unity gain loop. How can oscillation be generated ? Explain three-stage ring oscillator. 20

Or

6. (a) Discuss the mathematical model of voltage controlled oscillator. 10
(b) Explain the block diagram of simple phase lock loop. 10

Unit - IV

7. (a) Design and explain positive edge triggered D flip-flop. 10
(b) Explain the architecture of programmable logic array (PLA) with a neat diagram. 10

Or

8. Write short notes on the following : 20
(a) Serial Access Memory
(b) Content Addressable Memory

Unit - V

9. (a) Design a 4-bit adder/subtractor using data path operator. 10

P. T. O.

[4]

- (b) Design the following circuits : 10
- (i) 8-bit one/zero detector
 - (ii) 4-bit comparator

Or

10. (a) Design a 4×4 array multiplier. 10
- (b) Design and explain 3-bit incrementor circuit. 10