

Total No. of Questions : 5 ] [ Total No. of Printed Pages : 4

Roll No. ....

## CS/IT-304

**B. E. (Third Semester) EXAMINATION, June, 2009**

(New Scheme)

(Common for CS & IT Engg.)

**ELECTRONIC DEVICES AND CIRCUITS**

*Time : Three Hours*

*Maximum Marks : 100*

*Minimum Pass Marks : 35*

**Note :** Attempt *one* question from each Unit. All questions carry equal marks. Assume any missing data.

### Unit – I

1. (a) Define the following in MOSFET : 10
- (i) Subthreshold conduction
  - (ii) Channel length modulation
  - (iii) Hot carrier effect
  - (iv) Threshold voltage
- (b) Describe the basic operation of an enhancement type MOSFET. 10

*Or*

- (a) Explain the hybrid parameters with equivalent circuit. 10

**P. T. O.**

- (b) If a silicon transistor in fig. 1 has a minimum value of  $h_{fe} = 30$ , find the output levels for input levels of 0 and 10 volts. 10

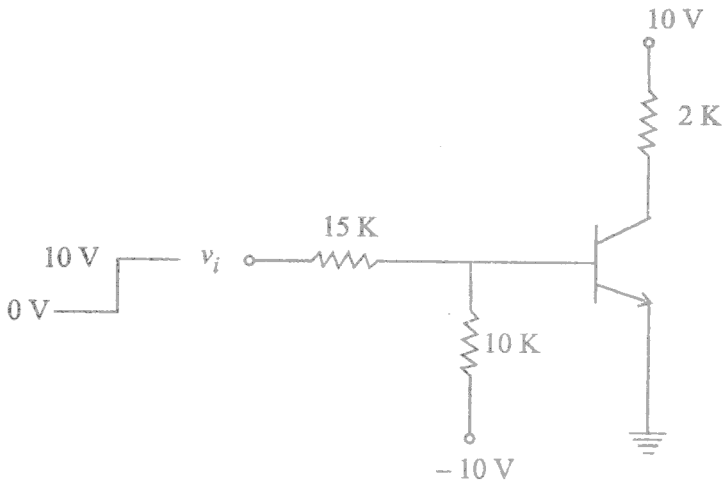


Fig. 1

## Unit – II

2. (a) Explain the following terms : 10  
 (i) Characteristics of negative feedback  
 (ii) Harmonic distortion  
 (b) Explain the working of RC coupled transistor amplifier in CE configuration. 10

Or

- (a) Discuss various types of distortions associated with amplifiers. 10  
 (b) Show that the maximum conversion efficiency of the idealized Class B push-pull limits is 78.5%. 10

## Unit – III

3. (a) Define the following terms : 8  
 (i) CMRR  
 (ii) Slew rate

- (iii) Offset voltage
- (iv) Impedance
- (b) Design a bandpass filter as shown in fig. 2, with a centre frequency  $f_c = 1$  kHz and  $Q = 5$ ,  $A_f = 8$ . Next, find the change in  $R_3$  when centre frequency is changed to 2 kHz, keeping  $A_f$  and  $B_w$  constant. 12

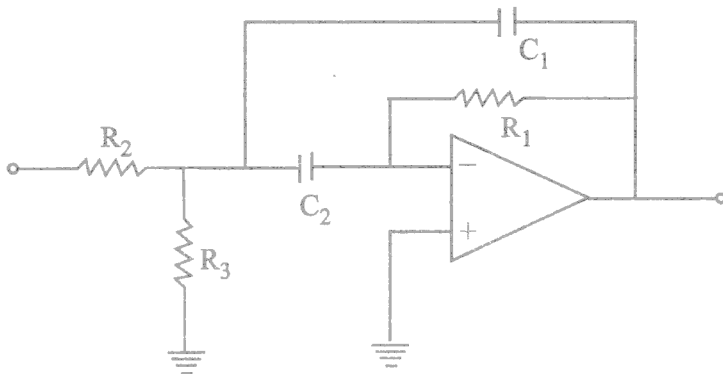


Fig. 2

Or

- (a) Discuss the Instrumentation Amplifier using OP-AMP. 10
- (b) Explain the working of an astable multivibrator using 555 timer. 10

#### Unit – IV

- 4. (a) List different types of oscillator with their applications. 10
- (b) Explain the biasing of power amplifier and write its applications. 10

Or

- (a) Explain Darlington amplifier. 10

P. T. O.

[ 4 ]

- (b) Write the application of 555 timers. Explain the circuit of V to F converter. 10

**Unit – V**

5. (a) What do you mean by Regulation ? Explain with the help of block diagram of regulator circuit. 10  
(b) Differentiate the function of SMPS and UPS. 10

*Or*

Write short notes on any *two* of the following : 20

- (i) Shunt regulators
- (ii) Current to Voltage converter
- (iii) Bootstrapping