

UNIT - V

9. Discuss and compare the following methods for synchronous motor control
- Separate control
 - Self control

OR

10. Explain the following operation of synchronous motor drive fed from a UFI.
- Open loop control
 - Closed loop control

RGPVONLINE.COM

Roll No

EX - 802(NGS)**B.E. VIII Semester**

Examination, June 2014

Electrical Drives**Time : Three Hours****Maximum Marks : 70****Note :** All Questions carry equal marks.**UNIT-I**

- Explain the working of a single phase fully controlled converter fed separately excited D.C. motor drive and derive the relevant mathematical expression for continuous conduction mode.
 - A 200V, 875 rpm, 150 amps separately excited d.c motor has an armature resistance of 0.06Ω . It is fed from a single phase fully controlled converter rectifier with an a.c source voltage of 220V, 50HZ. Assuming continuous conduction calculate
 - Firing angle for rated motor torque and 750 rpm.
 - Motor speed for $\alpha = 160^\circ$ and rated torque.

OR

- With relevant wave forms discuss the operation of three phase fully controlled converter fed separately excited D.C motor drive.

- b) Discuss rectifier control of D.C series motor drive fed from a single phase half controlled converter. Derive the mathematical expression required for plotting of speed torque characteristics.

UNIT-II

3. a) Explain multiquadrant operation of separately excited D.C motor drive fed from a dual converter.
- b) A 220V, 1500 rpm, 50 A, separately excited D.C motor with armature resistance of 0.5Ω is fed from a circulating current. Dual converter with three phase a.c source voltage of 165V (line). Determine converter firing angle for the following operating points
- Motoring operation at rated motor torque and 1000 rpm.
 - Braking operation at rated motor torque and -1000 rpm.

OR

4. a) Discuss the operation of a four quadrant chopper fed variable speed reversible D.C series motor drive. Derive the relevant mathematical expression.
- b) A 230V, 1200 rpm, 15 A separately excited D.C motor has an armature resistance of 1.2Ω motor is operated under dynamic braking with chopper control. Braking resistance has a value of 20Ω .
- Calculate duty ratio of chopper for motor speed of 1000 rpm and braking torque equal to 1.5 times rated motor torque.

UNIT-III

5. Give reasons for the following
- Why stator voltage control is suitable for speed control of induction motor drive in fan and pumps.
 - Stator voltage control is an inefficient method of induction motor speed control.

OR

6. For variable frequency control of induction motor drive explain the following points.
- For speeds below base speed (V/δ) ratio is maintained constant.
 - For speeds above base speed terminal voltage is maintained constant.

UNIT-IV

7. a) Compare the operation of VSI and CSI fed induction motor drive.
- b) With the help of relevant mathematical derivation and waveforms, explain the operation of static scherbius drive.

OR

8. Discuss static rotor resistance control scheme of induction motor drive.