

Roll No.

RGPVONLINE.COM

EX-405(N)

B. E. (Fourth Semester) EXAMINATION, June, 2010

(New Scheme)

(Electrical & Electronics Engg. Branch)

ELECTRONIC DEVICES AND CIRCUITS – II

[EX-405(N)]

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt *one* question from each Unit. All questions carry equal marks.

Unit – I

1. (a) Discuss the design aspects of monolithic op-amps.
- (b) Explain the working principle of Astable multivibrator using op-amp.

Or

2. (a) Discuss the frequency compensation techniques.
- (b) Explain the working principle of logarithmic amplifier.

Unit – II

3. (a) What are active filters ? Explain the principle of working of HPF. RGPVONLINE.COM
- (b) Explain the working principle of Bistable multivibrator using 555 timer.

P. T. O.

[2]

Or

4. (a) Explain the working of 556 IC as function generator.
- (b) Explain the principle of working of PLL IC.

Unit – III

5. (a) Explain the working principle of ribbon type microphones.
- (b) Explain the working of multiway speaker system.

Or

6. (a) Explain the cross over network and their frequency characteristics.
- (b) Discuss the disk and crystal recording technique.

Unit – IV

7. (a) Explain the working principle of Klystron amplifier.
- (b) Explain the working of backward wave oscillator.

Or

8. Write short notes on the following :
 - (i) IMPATT
 - (ii) LASER

Unit – V

9. (a) Explain the working of NAND gate using DTL logic family.
- (b) Explain the use of FET as a switch.

Or

10. (a) Discuss the characteristic of TTL with Schottkey devices.
- (b) Explain the transfer characteristic of CMOS logic gates.

EX-405(N)

5720