

Total No. of Questions : 10 ] [ Total No. of Printed Pages : 3

Roll No. ....

**401(O)**

**B. E. (Fourth Semester) EXAMINATION, Dec., 2009**

**(Old Scheme)**

**(Common for EC/EI & BM Engg.)**

**ELECTRONICS – II**

*Time : Three Hours.*

*Maximum Mark : 100*

*Minimum Pass Marks : 35*

**Note :** Attempt *one* question from each Unit. All questions carry equal marks. Total *five* questions are to be attempted.

**Unit – I**

1. (a) Draw the circuit diagram of differential amplifier and derive expressions for common mode gain and CMRR.
- (b) Draw and explain the transfer characteristics of DIFF Amplifier. Over what differential voltage is the DIFF AMP a good limiter ?

*Or*

2. (a) Analyse differential amplifier circuit using *h*-parameters.
- (b) Draw and explain current mirror circuit.

**P. T. O.**

**Unit – II**

3. (a) Explain the following regarding Op-Amp :
- (i) Slew rate
  - (ii) Input offset voltage
  - (iii) Bias and offset currents
- (b) Draw the circuit diagram of Schmitt trigger and find the expression for threshold voltages. Also give its applications.

*Or*

4. (a) What are the characteristics of an ideal Op-Amp ? Explain the working of Op-Amp in inverting and non-inverting mode.
- (b) Draw the circuit diagram of instrumentation amplifier and differentiator circuit using Op-Amp and derive the expressions for output voltage.

**Unit – III**

5. (a) Design a band pass second order Butterworth filter with the following specifications :
- Lower cut-off frequency  $F_L = 200 \text{ Hz}$
- Upper cut-off frequency  $F_H = 1 \text{ kHz}$
- Pass Band gain = 4
- (b) Using 555 timer draw the circuit of monostable multivibrator and find the expression for pulse width.

*Or*

6. (a) Design and explain second order low pass filter with its high cut-off frequency = 5kHz and pass band gain = 4.

- (b) With the help of circuit diagram explain V/F and F/V converters.

**Unit – IV**

7. (a) Explain the working principle of moving coil type microphone. Also draw the constructional details and equivalent circuit.
- (b) Explain in brief different types of loudspeakers and their characteristics.

*Or*

8. (a) Explain the working of Ribbon microphone. Also define the term sensitivity and noise figure for a microphone.
- (b) Discuss in brief various types of sound recording system. What is reverberation ?

**Unit – V**

9. (a) Explain two transistor analogy for SCR. Also explain its VI characteristics.
- (b) Draw and explain the behaviour of switching characteristics of a thyristor during its turn on and turn off process.

*Or*

10. (a) Explain and draw circuits for gate triggering and firing circuit using UJTs.
- (b) What is the use of flywheel diode ? Explain with circuit diagram and wave forms.

