

Unit-V

Roll No

EX - 504**B.E. V Semester**

Examination, June 2015

Power Electronics Devices and Circuits**Time : Three Hours****Maximum Marks : 70**

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
 ii) All parts of each questions are to be attempted at one place.
 iii) All questions carry equal marks, out of which part A and B (Max.50 words) carry 2 marks, part C (Max.100 words) carry 3 marks, part D (Max.400 words) carry 7 marks.
 iv) Except numericals, Derivation, Design and Drawing etc.

Unit-I

1. a) What is the necessity for connecting power semiconductor devices in series? What are the precautions to be taken in such condition?
- b) Discuss the over voltage and dv/dt protection of power semiconductor devices.
- c) Sketch the turn-off characteristics of an SCR and there from explain the turn-off mechanism.
- d) What are the various methods of turn-on of SCRs, explain?

OR

Following are the specifications of a thyristor operating from a supply of peak voltage 500V. Repetitive peak current rating of SCR, $I_p = 250A$. Also,

5. a) What is a cycloconverter? Discuss its principle.
- b) Draw the circuit diagram voltage and current waveform of single phase full wave voltage controller with resistive load.
- c) List the advantage and disadvantages of Back and Boost regulators.
- d) The single phase full-wave controller has a resistive load of 1.5Ω with input voltage 120V at 50Hz. If the desired output power is 7.5 kW. Determine
 - i) Firing angles of thyristors
 - ii) rms output voltage
 - iii) Input power factor

OR

Discuss the operation of Cuk converter with the help of a circuit diagram and voltage and current waveforms.

$$\left(\frac{di}{dt}\right)_{Max} = \frac{60A}{\mu s}; \left(\frac{dVa}{dt}\right)_{Max} = \frac{200V}{\mu s}$$

Take a suitable factor of safety for these specifications mentioned above. Design a suitable a suitable snubber circuit if the minimum load resistance is 20Ω . Take $r = 0.65$.

Unit-II

2. a) Explain the effect of freewheeling diode.
- b) The half wave circuit is supplied at 120V line to neutral. Determine the average load voltage for firing angle 0° , assuming the load current to be continuous and level with a constant 2.5V drop on each thyristor.
- c) Discuss the effect of source inductance on the performance of a single phase fully controlled converter, indicating clearly the conduction of various thyristor during one cycle.
- d) Explain the operation of a three phase fully-controlled bridge converter with inductive load. Draw the voltage and current wave forms for $\alpha = 70^\circ$. List the firing sequence of SCRs.

OR

Three phase half-wave rectifier consists of a resistance and a very large inductance. The inductance is so large that the output current I_d can be assumed to be continuous and ripple free. For $\alpha = 60^\circ$

- i) Determine average value of output voltage if phase voltage, $V_p = 120V$.
- ii) Draw the waveforms of output voltage and output current.

Unit-III

3. a) Explain the principle of operation of an inverter.
- b) Compare between voltage source and current source inverter.
- c) Why voltage control is needed in inverter circuits? State the various methods of voltage control in inverter circuits.
- d) Draw and explain the operation of 1- ϕ McMurray - Bedford full bridge inverter circuit. Also draw the related voltage and current waveform.

OR

Draw and explain the operation of three-phase series inverter circuit. State the limitation of this inverter.

Unit-IV

4. a) Draw the schematics of step-up and step-down choppers.
- b) Give the classification of chopper commutation.
- c) With the help of voltage and current waveforms, explain the working of first quadrant chopper.
- d) Describe a Morgan chopper with associated voltage and current waveforms. Enumerate the demerits of Morgan chopper compared to Jones chopper.

OR

A step-up chopper has input voltage of 220V and output voltage of 660V. If the non-conducting time of thyristor is 100μ sec. Compute the pulse width of output voltage. If the pulse width is halved for a constant frequency operation, find the new output voltage.