

Total No. of Questions : 10] [Total No. of Printed Pages : 3

Roll No.

EC-403

B. E. (Fourth Semester) EXAMINATION, June, 2009

(New Scheme)

(Electronics & Communication Engg. Branch)

DIGITAL ELECTRONICS

(EC – 403)

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt any five questions. All questions carry equal marks.

Unit – I

1. (a) Convert the following : 10
 - (i) $[1001011]_{\text{gray}} = [\quad]_2$
 - (ii) $[10110110 \cdot 0011]_2 = [\quad]_{\text{BCD}}$
 - (iii) $[10110101]_{2421} = [\quad]_{10}$
 - (iv) $[57621]_8 = [\quad]_{16}$
 - (v) $[76]_{10} = [\quad]_{\text{gray}}$
- (b) Simplify the following : 5
 - (i) $Y = AB + \overline{AC} + \overline{ABC} (AB + C)$
 - (ii) $Y = \overline{\overline{AB + ABC + A(B + AB)}}$
- (c) Using K map simplify the following function : 5
$$f(a, b, c, d) = \Sigma (0, 1, 6, 8, 9, 12, 13) + \Sigma_d (4, 10, 14)$$

P. T. O.

Or

2. (a) Realise the function

$$Y = (A + C)(A + \overline{D})(A + B + \overline{C})$$

using NOR gates.

5

- (b) Realise the function $Y = \overline{AB} + A + (\overline{B + C})$ using NAND gates.

5

- (c) Find the minimal sum of products for the Boolean expression $f = \Sigma (1, 2, 3, 7, 8, 9, 10, 11, 14, 15)$ using the Quine-McCluskey method.

10

Unit – II

3. (a) Explain the working of 4-bit serial adder/subtractor.

10

- (b) Implement the function $F(A, B, C, D) = \Sigma (0, 1, 3, 4, 8, 9, 15)$ using multiplexers.

10

Or

4. (a) Explain the look ahead carry generator and discuss its utility in adders.

10

- (b) Design a BCD to excess-3 converter with a BCD to decimal decoder and four OR gates.

10

Unit – III

5. (a) Explain the working of Monostable multivibrator using 555 timer.

10

- (b) Discuss the race around condition in J-K flip-flop and how it could be eliminated ?

10

Or

6. Design a MOD-12 binary counter using J-K flip-flop.

20

Unit – IV

7. (a) Explain the organisation and construction of RAM BUS ROM. 10
- (b) Design a combinational circuit that gives a binary output equal to the square of binary code decimal number 0 through 9 using diode matrix. 10

Or

8. (a) With the help of logic diagram and circuit diagram explain static RAM cell. 10
- (b) Explain the working of PAL. 10

Unit – V

9. (a) With the help of circuit diagram explain the working of HTL Nand gate. Also discuss the advantages and disadvantages of HTL family. 10
- (b) With the help of basic circuit of TTL NAND gate explain tristate output. 10

Or

10. (a) Explain the principle of IIL logic family. 10
- (b) Explain the working of NAND gate using *n*-channel MOS logic circuits. 10