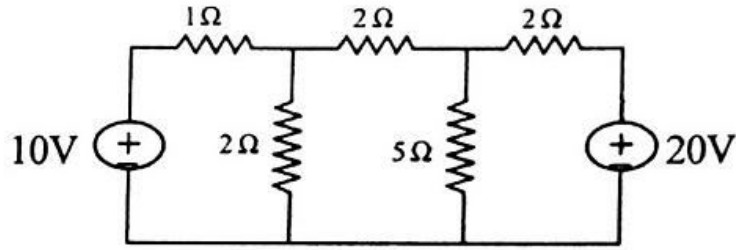


BE - 104  
B.E. I & II Semester Examination, December 2013  
Basic Electrical & Electronics Engineering  
Time : Three Hours  
Maximum Marks : 70

note: Attempt all the questions. Every question has internal choice.

1. a) State and explain superposition theorem.
- b) Calculate current through 5 ohm resistance using loop analysis.



OR

2. a) Define the following: 7
  - i) Average value of AC voltage
  - ii) RMS value of AC voltage
  - iii) Power factor
  - iv) Active power
  - v) Reactive power
  - vi) Apparent power
  - vii) Three phase balanced supply.
- b) A coil of resistance 100 and inductance 0.1H is connected in series with 150pF capacitor across a 200V, 50Hz supply calculate: 7
  - i) Inductive reactance
  - ii) Capacitive reactance
  - iii) Impedance
  - iv) Current
  - v) Power factor
  - vi) Voltage across the coil
  - vii) Voltage across capacitor.
3. a) Derive EMF equation for single phase transformer 7
- b) A single phase transformer is connected across 200V, 50Hz. supply. Number of turns in primary is 500 while in secondary is 1000. the net cross sectional area of the core is 80cm<sup>2</sup>= calculate:
  - i) Transformation Ratio.
  - ii) Maximum flux density
  - iii) EMF induced in secondary winding 7

OR

4. a) What quantities can be find out using open circuit test on I b transformer. Explain how you can perform open circuit test on lep transformer in the laboratory. 7  
b) A 100 KVA, 1000/10,000 V, 50Hz single phase transformer has an iron loss of 1100 w the copper loss. With 5A in the high. Voltage winding is 400W. Calculate efficiency at 100% normal load for p.f. 1.0 and 0.8. 7
5. a) Describe the constructional details of d.c. machine giving; suitable diagram. 7  
b) What do you mean by separately excited and self excited d.c. generator sketch following type of d.c. generator. 7
- i) Shunt wound
  - ii) Series wound
  - iii) Compound generator
- OR
6. Draw and explain Torque - slip characteristic of 3-phase induction.
7. a) State and prove Demorgan's theorem.  
b) Write and explain truth table of
- i) NAND gate
  - ii) EX-OR gate.
- OR
8. a) Draw and explain with the help of truth table working of J-K flip-flop.  
b) Draw and explain 4 bit full adder circuit.
9. Explain operation of PN junction diode when it is :
- i) Forward biase [RGPVONLINE.COM](http://www.rgpvonline.com)
  - ii) Reverse biase
- OR
10. a) Explain the working of Transistor when it is operated in CE mode.  
b) Explain in short application of transistor.