

Or

8. (a) Explain the need of Bootstrapping. How is it done ?
 (b) Differentiate on the basis of the performance of transformer coupled, RC coupled and direct coupled amplifiers.

Unit – V

9. Discuss the following applications of op-amp. :
 (i) Integrator
 (ii) Schmitt trigger
 (iii) Log amplifier

Or

10. Discuss the following applications of op-amps. :
 (i) Differentiator
 (ii) Instrumentation amplifier
 (iii) Antilog amplifier

Total No. of Questions : 10] [Total No. of Printed Pages : 4

Roll No.

EC-404

B. E. (Fourth Semester) EXAMINATION, Dec., 2011

(Electronics & Communication Engg. Branch)

ELECTRONIC CIRCUITS

(EC-404)

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt *one* question from each Unit. All questions carry equal marks.

Unit – I

1. (a) Determine the following for fixed bias configuration of fig. 1.

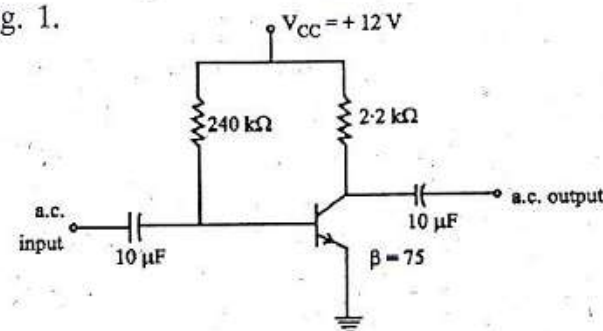


Fig. 1

- (i) I_{BQ} & I_{CQ} (ii) V_{CEQ}
 (iii) V_B & V_C (iv) V_{BC}
 (b) Analyse the common collector configuration using h -parameters.

Or Rgpvonline.com

2. (a) Determine the d. c. bias voltage V_{CE} and the current I_C for the voltage divider configuration of fig. 2.

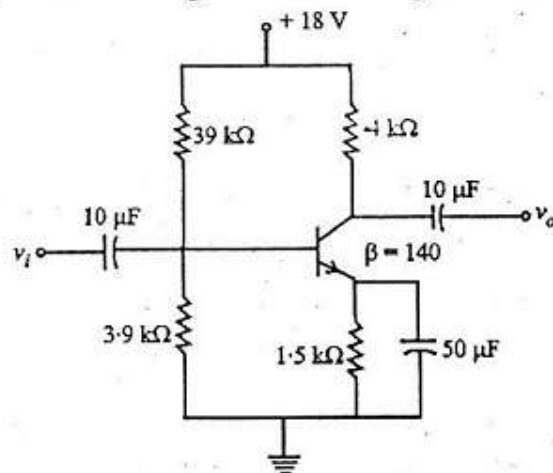


Fig. 2

- (b) Discuss what is Miller capacitance and its effects on voltage gain.

Unit – II

3. (a) Calculate the voltage gain of the circuit of fig. 3.

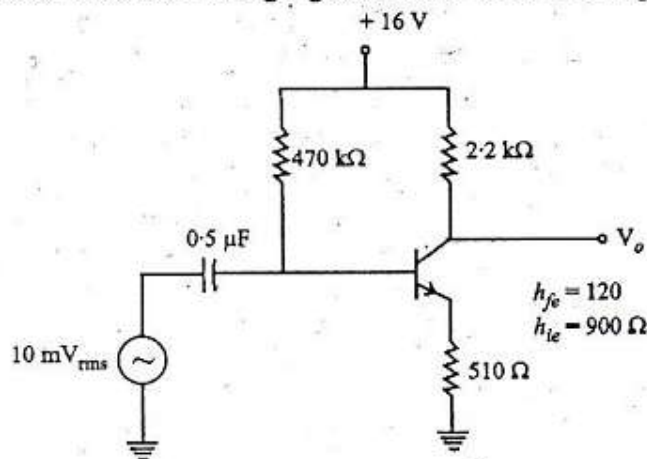


Fig. 3

- (b) Discuss the principle of working of Hartley oscillator.

Or

4. (a) Determine the feedback gain of a voltage series feedback FET amplifier shown in fig. 4.

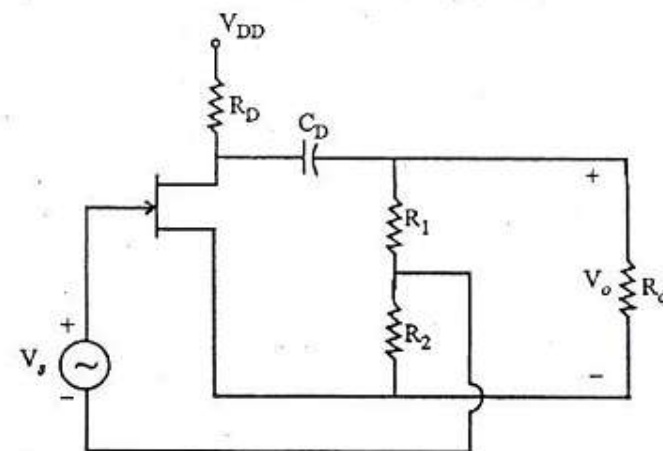


Fig. 4

- (b) Discuss the principle of working of RC phase shift oscillator.

Unit – III

5. (a) Determine the maximum efficiency of series fed Class A amplifier.
(b) Discuss the working of stagger tuned power amplifier.

Or

6. (a) For a Class B amplifier using a supply of $V_{CC} = 30$ V and driving a load of 16Ω , determine the maximum input power, output power and transistor dissipation.
(b) Discuss the effect of loading on power amplifier.

Unit – IV

7. (a) Discuss the effect of cascading on the bandwidth of amplifiers.
(b) Explain the working of differential amplifier and also calculate the differential and common mode gain.