

Roll No.....

**MEVD-103****M.E./M.Tech. I Semester**

Examination, December 2017

**Advanced Logic Design***Time : Three Hours**Maximum Marks : 70***Note:** i) Answer any five questions.

ii) All questions carry equal marks.

1. a) Design the minimum-cost product-of-sums expression for the function

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 4, 5, 6, 7, 8, 10, 12, 14, 15)$$

- b) Find the simplest realization of the function

$$f(x_1, \dots, x_4) = \sum m(0, 3, 4, 7, 9, 10, 13, 14), \text{ assuming that the logic gates have a maximum fan-in of two.}$$


2. a) Use functional decomposition to find the best implementation of the function

$$f(x_1, \dots, x_5) = \sum m(1, 2, 7, 9, 10, 18, 19, 25, 31) + D(0, 15, 20, 26)$$

How does your implementation compare with the lowest-cost SOP implementation? Give the costs.

- b) Show that the following distributive-like rule is valid:

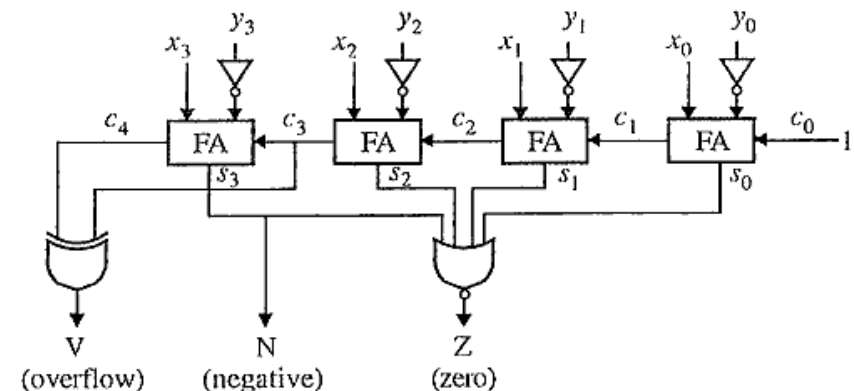3. a) Prove the validity of the expression  $\text{Overflow} = c_n \oplus c_{n-1}$  for addition of n-bit signed numbers.
- b) Determine the number of gates needed to implement an eight-bit carry-lookahead adder assuming that the maximum fan-in for the gates is four.
4. a) Prove that the XOR operation is associative, which means that  $x_i \oplus (y_i \oplus z_i) = (x_i \oplus y_i) \oplus z_i$ .
- b) Write Verilog code to specify the circuit in Figure (Comparator Circuit) 4.1




5. a) Implement the function

$$f(w_1, w_2, w_3, w_4, w_5) = \bar{w}_1 \bar{w}_2 \bar{w}_4 \bar{w}_5 + w_1 w_2 + w_1 w_3 + w_1 w_4 + w_3 w_4 w_5$$

by using a 4-to-1 multiplexer and as few other gates as possible. Assume that only the uncomplemented inputs  $w_1, w_2, w_3, w_4$  and  $w_5$  are available.

- b) Write Verilog code for a 4-to-2 binary encoder.

 6. a) A universal shift register can shift in both the left-to-right and right-to-left directions, and it has parallel-load capability. Draw a circuit for such a shift register.
- b) Derive the state diagram for an FSM that has an input  $w$  and an output  $z$ . The machine has to generate  $z = 1$  when the previous four values of  $w$  were 1001 or 1111; otherwise,  $z = 0$ . Overlapping input patterns are allowed.
7. a) Design a synchronous sequential circuit whose state diagram is shown in Figure. The type of flip-flop to be use is J-K.



- b) Design a clocked synchronous state machine with two inputs,  $X$  and  $Y$  and one output,  $Z$ . The output should be 1 if the number of 1 input on  $X$  and  $Y$  since reset is a multiple of 4 and 0 otherwise.
8. a) Derive a hazard-free minimum-cost SOP implementation for the function
- $$f(x_1, \dots, x_5) = \sum m(2, 3, 14, 17, 19, 25, 26, 30) + D(10, 23, 27, 31).$$
- b) Explain the metastability problem and its solution.