

Roll No

EX - 405**B.E. IV Semester Examination, June 2014
Electronic Devices and Circuits - II****Time : Three Hours****Maximum Marks : 70**

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
 ii) All parts of each question are to be attempted at one place.
 iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks.
 iv) Except numericals, Derivation, Design and Drawing etc.

- 1) a) Draw the frequency response characteristics of a typical op-amp. 2
- b) What is a precision diode? Explain with suitable example? 2
- c) Draw the circuit of an emitter coupled differential amplifier. Explain why the CMRR $\rightarrow \infty$ for a symmetrical circuit with $R_e \rightarrow \infty$. 3
- d) Explain the operation of square wave generator using op-amp with capacitor and output voltage waveforms. How can you obtain a non-symmetrical square wave? 7

OR

Design a square wave oscillator for $f_o = 1\text{KHz}$ using op-amp 741 and a d.c. supply voltage of $\pm 12\text{V}$.

- 2) a) Explain the wide band pass filter with the help of circuit diagram. 2
- b) Explain the switched capacitor filter in detail. 2
- c) Design a band pass second order Butter worth filter with following specification -
 Lower cut-off frequency $f_L = 200\text{Hz}$
 Upper cut-off frequency $f_H = 1\text{KHz}$
 Pass band gain = 4
 Also calculate the value of Q. 3
- d) Write a short note on phase locked ICs (PLL) and their application. 7

OR

Draw the pin diagram of 555 timer and also explain function of each pin in detail.

- 3) a) Explain moving coil microphone with its working principle. 2
- b) Explain the working of a condenser microphone. 2
- c) With the help of neat diagram explain the principle of working of a ribbon microphone. 3
- d) Discuss in detail of various types of sound recording system. 7

OR

What do you understand by reverberation? Explain the importance of reverberation.
 Write down the Sabine's equation for reverberation timer and define the terms used.

- 4) a) Explain in detail about TUNNETT diode. 2
 b) Explain the Gunn Effect using two valley theory. 2
 c) Describe the construction and principle of operation of a reflex Klystron with its applications. 3
 d) What do you mean by Maser's? Explain the principle of ruby Maser's with its applications and characteristics. 7

OR

Explain in detail of backward diode? An IMPATT diode has a drift length of $8\mu\text{m}$. Determine the drift time of a carrier and operating frequency.

- 5) a) Explain briefly the characteristics of MOS logic. 2
 b) Explain the purpose of the totem pole output stage used in a TTL gate. 2
 c) The MOS transistor is bilateral i.e. current may flow from source to drain or from drain to source. Using this property, derive a circuit that implements the Boolean function. $Y = \overline{(AB + CD + AED + CEB)}$ 3
 d) Explain the switching characteristics of CMOS. Also explain the rise time and fall time in CMOS gates. 7

OR

Explain the following

- i) MOS inverter
 ii) CMOS inverter