

Total No. of Questions : 8]

[Total No. of Printed Pages : 2

Roll No


EC-605 (GS)**B.E. VI Semester**

Examination, May 2018

Grading System (GS)**VLSI Circuits and Systems****Time : Three Hours****Maximum Marks : 70**

- Note: i) Attempt any five questions.
 ii) All questions carry equal marks.
 iii) Assume any missing data.

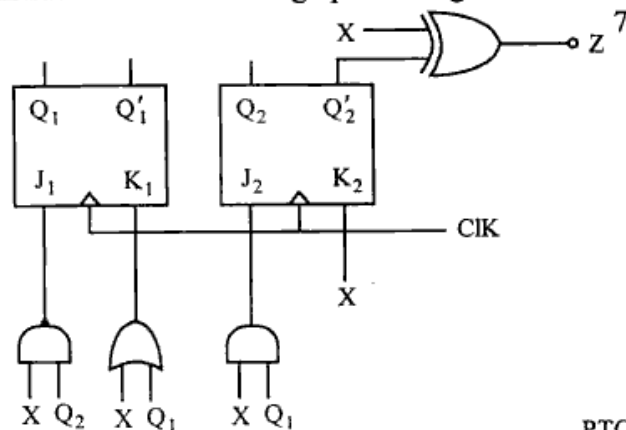1. a) What do you know about the following domain elaborate in a proper fashion. 7
 - i) Behavioural domain rgpvonline.com
 - ii) Structural domain
 - iii) Geometrical layout domain
- b) Implement following digital function using CMOS gate
 - i) $Y = a + bc'$
 - ii) $Y = (a+b) \cdot (c+d) \cdot e'$7
2. a) Construct a stable table and graph for the given network. 7



EC-605 (GS)

PTO

[2]

- b) Define a "strongly connected sequential machine" and illustrate the same with example. 7
3. a) Find the hazard free realization of the following function $F(A, B, C, D) = \sum_m (0, 2, 6, 7, 8, 10, 12, 13)$ 7
- b) Boolean expression for the circuit is given by following equations. 7

$$Y_1 = x_1' x_2 + x_2 y_1$$

$$Y_2 = x_1 y_2 + x_2$$
 find flow table for the circuit.
4. a) How an SM chart can be realize by using a MUX and PLA. 7
- b) Draw the ASM chart of a sequence recognizer to recognize the input sequence of pairs $xy = 11, 01, 11, 00$. 7
5. a) Design a Binary to Gray code converter using 7
 - i) PROM
 - ii) PLA
 - iii) PAL
- b) How ROM's can be used to implement combinational circuits? 7
6. a) Explain the basic principles of the path-sensitization method. 7
- b) Differentiate between struck-at-zero and struck-at-one fault. 7
7. a) Explain the state assignments using partitions. 7
- b) Design a sequence detectors which produces a output '1' on 10010 sequence, otherwise zero output. 7
8. Briefly explain the following. 14
 - a) Inflammation Loss-less machines
 - b) FPGA technologies
 - c) Test Vector

EC-605 (GS)