

Roll No

EC-3002 (CBGS)**B.E. III Semester**

Examination, December 2017

Choice Based Grading System (CBGS)**Digital Circuits and System***Time : Three Hours**Maximum Marks : 70*

- Note:** i) Attempt any five questions.
ii) All questions carry equal marks.

1. a) What is universal gate? Implement AND, OR and NOT gates using NAND gates and NOR gates.
b) Convert (47)₁₀ to
i) Binary
ii) Octal
iii) Hexadecimal
2. a) Explain the following classification on binary codes.
Weighted codes
Non-weighted codes
Reflective codes
Alphanumeric codes
b) Write De-Morgan's theorem. Find the complement of the functions
 $F_1 = x'yz' + x'y'z$ and $F_2 = x(y'z' + yz)$. By applying De-Morgan's theorem.

3. a) Design a full adder circuit and write its truth table. Implement it with logic gates.
b) Define multiplexers and draw a 4×1 multiplexer. How many selection lines are there?
4. a) Implement a full adder circuit with a (3 to 8 line) decoder and two OR gates.
b) Simplify the Boolean function using K map.
 $F(ABCD) = \text{sum of } (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
5. a) Differentiate combinational and sequential circuits. Give suitable examples for each class.
b) What do you mean by Flip-Flops? Define D flip-flop with diagrams and tables.
6. a) Differentiate the followings:
i) Synchronous and asynchronous counters
ii) Dynamic and static RAM
b) What do you mean by shift registers? Design a shift left register of 4 bits.
7. a) Differentiate TTL and DTL logic families. Define fanout.
b) Define the terms PROM, EEPROM, EAPROM.
8. Write short notes on any two:
a) PLA
b) ECL family
c) Ring counter
d) Exclusive OR gate

179