

Roll No

CS/IT - 304**B.E. III Semester**

Examination, June 2015

Electronics Devices and Circuit**Time : Three Hours****Maximum Marks : 70**

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
- ii) All parts of each question are to be attempted at one place.
- iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks.
- iv) Except numericals, Derivation, Design and Drawing etc.

1. a) Draw V-I characteristic of P-N junction silicon diode.
- b) Explain the diode current equation.
- c) For a CE circuit shown in figure (1) Calculate the values of I_B , I_C , I_E , and V_{CE} . Assume $\beta = 50$ and neglect V_{BE} .

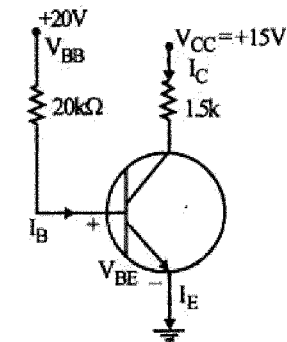


Fig. 1

[2]

- d) Explain how zener diode working as a Voltage Regulator.

OR

For the circuit shown in figure (2) determine V_L , V_R , I_Z and P_2 .

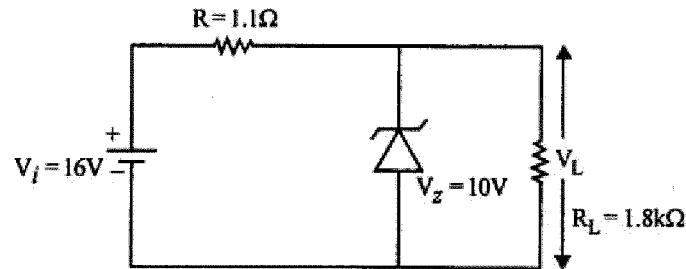


Fig. 2

2. a) Explain advantages of a Negative feedback in an amplifiers.
- b) Explain the Barkhausen criterion for oscillators.
- c) Draw the circuit diagram of Hartley oscillator.
- d) Explain the Wien's bridge oscillator using BJT. For this circuit calculate the frequency of oscillation.

OR

Discuss Class-B power amplifiers and calculate its overall efficiency.

3. a) In which region Transistor is working as a switch explain.
- b) Explain how diode is used as clipper.
- c) What are multivibrators?
- d) Draw and explain the working of bistable multivibrator.

OR

Draw the circuit of a differential amplifiers and explain its operations.

[3]

4. a) Explain the characteristics of an ideal Op-Amp.
- b) What do you mean by virtual ground?
- c) Draw the circuit diagram of Op-Amp in inverted mode and write the formula for inverting amplifier.
- d) Explain with diagram how an operational amplifier can be used as an differentiator.

OR

Write a short notes on Schmitt trigger circuit.

5. a) Draw the block diagram of a Regulated Power Supply.
- b) Can diode be used as a Voltage Regulator?
- c) Draw the block diagram of SMPS.
- d) Explain fold back current limiting circuit.

OR

Explain the working of Series Regulator.
