

Roll No

EX-405 (Old)**B.E. IV Semester**

Examination, June 2016

Electronic Devices and Circuits - II*Time : Three Hours**Maximum Marks : 70*

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
 ii) All parts of each question are to be attempted at one place.
 iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks.
 iv) Except numericals, Derivation, Design and Drawing etc.

Unit - I

- Write the characteristics of ideal and practical op-amp.
 - Define slew rate and off-set voltage of op-amp.
 - Describe logarithmic amplifier using op-amp.
 - Explain frequency compensation techniques of operational amplifier.

OR

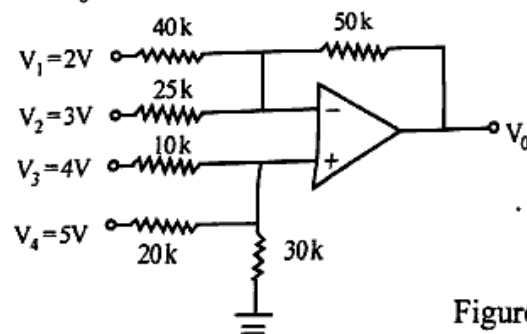
Find V_0 for the adder-subtractor shown in figure 1.1.

Figure 1.1

EX-405 (Old)

PTO

[2]

Unit - II

- Draw frequency response of active LPF and HPF.
 - Compare higher order and lower order filters.
 - Explain 555 timer and its applications.
 - Explain phase locked loop.

OR

Design a second order low pass filter at a high cut off frequency of 1 kHz.

Unit - III

- Define Acoustics.
 - Explain the working of moving coil microphone.
 - Explain noise figure and sensitivity.
 - Write a short note on sound recording systems.

OR

Explain cross over network and its frequency characteristics.

Unit - IV

- State the limitations of conventional tubes.
 - What is GUN effect?
 - Discuss the high frequency limitations of transistors.
 - Write the short notes on Klystron amplifier and magnetrons.

OR

Explain

- MASER and LASER
- IMPATT and TRAPATT
- TUNETT

Unit - V

- Explain transistor as a switch.
 - Compare ECL and TTL.
 - What are the advantages of CMOS circuits?
 - Explain TTL and its characteristics.

OR

Discuss the rise and fall time in CMOS gates.

EX-405 (Old)