

EE/EX-226

B.E. IV Semester

Examination, June 2017

Choice Based Credit System (CBCS)

Digital Electronics Logic Design

Time : Three Hours] [Maximum Marks : 60

Note: i) Attempt any five questions.

ii) All questions carry equal marks.

1. a) Calculate $A + B$, $A - B$, $A \times B$ and $A \div B$ for the following pairs of members.

i) 10101, 1011

ii) 372, 156

iii) 2CF3, 2B

iv) 1000, 777

b) Draw logic implementation of an inverter using two-input NOR.

2. a) Design a 4-bit decimal adder using 4-bit binary address. b) Implement the full subtractor using demultiplexer.

3. a) Explain the operation of master slave flip-flop and show how the race around condition is eliminated.

b) Explain the operation of JK flip-flop with neat diagram.

4. Design a 3-bit synchronous counter using D-flip-flop.

5. Implement the following Boolean function using 8×1 multiplexers

$$F(A, B, C, D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$$

6. a) Explain the principle working of sample and hold circuits.

b) Design a NAND gate using CMOS logic and explain its working.

7. a) Design a 4-bit Johnson counter.

b) What is ROM? Explain the meaning of (32×8) ROM and describe it.

8. Write a short notes on any two of the following:

a) PLA

b) V-F counter

c) Decoding glitches
