

Total No. of Questions : 10] [Total No. of Printed Pages : 4

Roll No.

BE-104(GS)

B. E. (First/Second Semester)

EXAMINATION, Dec., 2011

(Grading System)

(Common for all Branches)

**BASIC ELECTRICALS AND ELECTRONICS
ENGINEERING**

[BE-104(GS)]

Time : Three Hours

Maximum Marks : 70

Minimum Pass Marks : 22 (D Grade)

Note : Attempt *one* question from each Unit. All questions carry equal marks. Assume suitable data if necessary.

Unit-I

1. (a) What do you understand by dependent and independent sources ? Explain with neat sketches.
- (b) State superposition theorem. In the given network, making use of superposition theorem, determine the currents in resistors R_1 , R_2 and R_3 and also the currents in voltage source E .

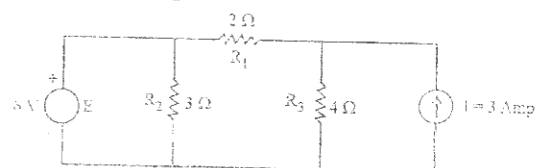


Fig. 1

P. T. O.

[2]

BE-104(GS)

Or

2. (a) Voltage $v(t) = v_0 \cos(\omega t + \phi)$ is applied to a series circuit containing resistor R , inductor L and capacitor C . Obtain expression for the steady state current.

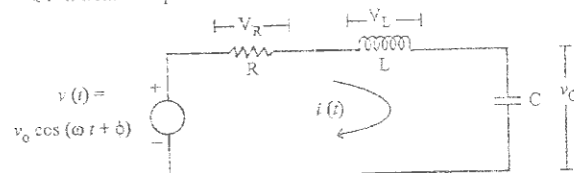


Fig. 2

- (b) Describe star connection method for interconnection of 3-phase supply.

Unit-II

3. (a) (i) State Faraday's law of electromagnetism.
 (ii) What is meant by turn ratio in transformer?
 (iii) What is magneto-motive force?
 (iv) Mention the two important electrical performances of transformer.
 (b) Explain the principle of operation of transformer with suitable sketches.

Or

4. (a) The O. C. and S. C. tests on a 5 kVA, 230/110 V, 50 Hz transformer gave the following data :
 O. C. test (H. V. side) — 230 V, 0.6 A, 80 W
 S. C. test (L. V. side) — 6 V, 15 A, 20 W
 Calculate percentage efficiency and regulation of a transformer on full load at 0.8 p. f. lagging.
 (b) Derive the condition for maximum efficiency of a transformer.

[3]

BE-104(GS)

Unit – III

5. (a) Derive the expression for generated voltage in D. C. machine.
(b) Draw and explain the construction of a single-phase induction motor with neat sketches.

Or

6. (a) Obtain an expression for e. m. f. equation of 3-phase induction motor.
(b) What are the different methods of speed control in D. C. motor ? Discuss in details.

Unit – IV

7. (a) Convert the following numbers into decimal :
(i) $(11111111)_2$
(ii) $(100)_8$
(iii) $(FFFF)_{16}$
(iv) $(01010101)_2$
(v) $(100.100)_2$
(b) Give the logic symbol and truth table for the following logic gates (any two) :
(i) NAND
(ii) NOR
(iii) NOT
(iv) EX-OR

Or

8. (a) Distinguish between combinational and sequential logic circuits giving example of each.
(b) Draw the circuit diagram of a half adder and derive its truth table.

R. T. O.

[4]

Unit – V

9. (a) (i) Name any *three* materials which are most widely used as semiconductors.
- (ii) What type of semiconductor results when silicon is doped with (a) donor impurities (b) acceptor impurities ?
- (iii) What is doping ?
- (iv) What is intrinsic semiconductor ?
- (v) What is operating points ?
- (b) Explain the forward and reverse bias operation and voltage-current characteristics of a PN junction diode.
- Or*
10. (a) Explain the working of Bipolar junction transistor in common emitter configuration.
- (b) Explain how a BJT can be used as (i) An amplifier (ii) 2 switch.

EE-104(GS)

45 (30)