

## EX-403(N)

B. E. (Fourth Semester) EXAMINATION, Dec., 2010

(New Scheme)

(Electrical & Electronics Engg. Branch)

DIGITAL ELECTRONICS LOGIC DESIGN --I

[EX-403(N)]


Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

**Note :** Attempt any *five* questions. All questions carry equal marks.

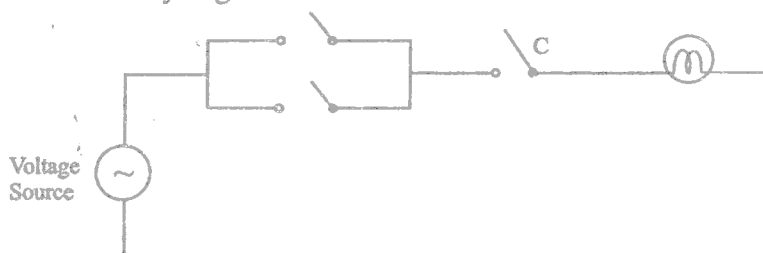1. (a) Express the following switching circuit given in figure in binary logic notation. 4



- (b) Perform conversions as below : 10

(i)  $(12.0625)_{16} \rightarrow ( )_2$

(ii)  $(10.1001)_2 \rightarrow ( )_{10}$

(iii)  $(1032.2)_4 \rightarrow ( )_{10}$

(iv)  $(2AC5.D)_{16} \rightarrow ( )_8$

(v)  $(225.225)_{10} \rightarrow ( )_{16}$

- (c) Explain the terms SOP, POS, Maxterms and Minterms in brief. 6

Or

2. (a) Reduce the equation to 3 literals :

$$[(CD)' + A]' + A + CD + AB \quad 3$$

- (b) Convert  $F(A, B, C, D) = \Sigma(0, 2, 6, 11, 13, 14)$  to other canonical form. 3

- (c) Show that the dual of Exclusive - OR is equivalent to its complement. 2

- (d) Simplify  $F(x, y, z) = \Sigma(2, 3, 6, 7)$ . 2

- (e) Add 647 and 487 in BCD. 3

- (f) What are gray codes ? Convert  $(1001010)_2$  to gray code. 5

- (g) Simplify  $F = \Sigma m(1, 2, 4, 5, 6, 10, 11, 14, 15)$  using K map. 2

3. (a) Implement a full adder circuit using multiplexers. 10

- (b) Implement the given function using NAND gates, assuming that both normal and complement inputs are available. 5

- (c) What are decoders ? Explain Obtain a  $4 \times 16$  decoder with two  $3 \times 8$  decoders. 5

Or

4. (a) What is a look ahead carry generator ? Explain. 10

- (b) A combinational circuit is defined as : 5

$$F_1(x, y) = \Sigma(0, 3)$$

$$F_2(x, y) = \Sigma(1, 2, 3)$$

Implement it using  $2 \times 4$  decoder.

- (c) Explain the working of a priority encoder. 5

5. (a) What is an RS flip-flop ? Explain with its logic diagram. Obtain its characteristic equation and truth table. 10
- (b) Design a sequential circuit with JK flip-flops to satisfy the following state equations : 10
- $$A(t+1) = A'B'CD + A'B'C + ACD + AC'D'$$
- $$B(t+1) = A'C + CD' + A'BC'$$
- $$C(t+1) = B$$
- $$D(t+1) = D'$$

Or

6. (a) What is a T flip-flop ? Explain separately how is it obtained from RS and JK flip-flops respectively. 10
- (b) Give three applications of flip-flops. Why triggering is required in flip-flops ? What are the different types of triggering ? Explain with example. Draw logic symbol for JK flip-flop with active low preset and clear. 10
7. (a) Draw the diagram of a MOD 8 ripple counter and waveforms at the output of flip flops. Why is it called a divide by 8 counter ? 10
- (b) Design a synchronous counter using flip-flops which counts in the strict sequence (1, 2, 3, 5, 7). 10

Or

8. (a) What is a shift register ? What are the different types of shift registers ? 10
- (b) Explain the working of a Johnson counter. 10
9. (a) Explain the working of a Ramp type A/D convertor. 10

[ 4 ]

- (b) What is a PLA ? What is the difference between ROM and PLA ? 10

*Or*

10. (a) What is a ROM ? Explain the different types of ROM. 10
- (b) What is a D/A convertor ? Explain R-2R D/A convertor. 10