

EX-405(N)

B. E. (Fourth Semester) EXAMINATION, Dec., 2010 (New Scheme)

(Electrical & Electronics Engg. Branch)

ELECTRONICS DEVICES AND CIRCUITS – II

[EX – 405(N)]

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt *one* question from each Unit. All questions carry equal marks. Assume suitable data if missing.

Unit – I

1. What is an op-amp. ? List *four* basic building blocks of an op-amp. and explain them.

Or

2. Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to about 1 kHz. If a sine wave of 1 volt peak at 1000 Hz is applied to the above designed differentiator, draw its output waveform.

Unit – II

3. Design a resonant RLC bandpass filter of figure shown below, with $f_o = 160$ Hz, 3-dB bandwidth, $B = 16$ Hz and the minimum input resistance seen by the voltage source V_s of $1\text{ k}\Omega$. Is this a practical circuit ?

Or

4. Draw the circuit diagram of a voltage to frequency converter using 555 timer and explain its working.

Unit--III

5. What do you understand by woofer, squawker and tweeter speakers ? Explain the necessity of cross-over networks.

Or

6. Describe the construction and principle of operation of the following :

- (i) Carbon microphone
- (ii) Moving coil loudspeakers

Unit—IV

7. Explain in detail the construction and operation of a two cavity klystron amplifier with the help of neat diagrams.

Or

8. Using energy band diagram, explain the tunnel diode characteristics point to point. Also list its applications.

Unit—V

9. Explain with neat diagrams the difference between TTL and DTL family.

Or

10. Write short notes on any *two* of the following :

- (i) CMOS inverter
- (ii) Interfacing BIT and CMOS gates
- (iii) FET and MOS switches