

Branch - EC

1

Total No. of Questions : 5] [Total No. of Printed Pages : 6

Roll No.

305(N)

B. E. (Third Semester) EXAMINATION, Feb., 2010

(New Scheme)

(Common for EC, EE, EI, EX & BM Engg. Branch)

NETWORK ANALYSIS

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt *one* question from each Unit. Total *five* questions are to be attempted. All questions carry equal marks.

Unit - I

1. (a) Explain clearly with the help of examples the following terms used in network analysis : 10
 - (i) Network graph
 - (ii) Tree of a graph
 - (iii) Cut-set and Tie-set matrix
- (b) Draw the dual for the network shown in fig. 1. 10

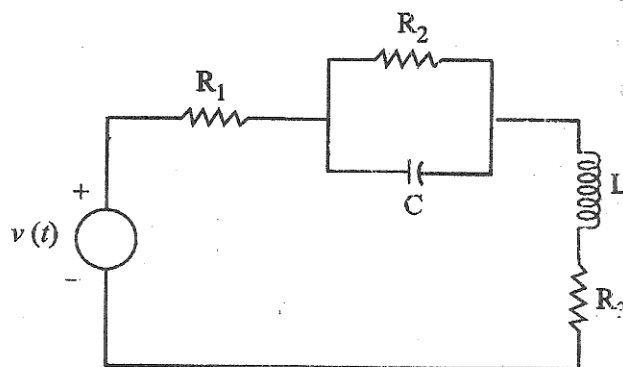


Fig. 1

P. T. O.

Or

- (a) Discuss the initial conditions of the elements inductor and capacitor. Outline the procedure for evaluating initial conditions in network problems. 8
- (b) In the network shown in fig. 2, the switch K is closed and a steady state is reached in the network. At $t = 0$, the switch is opened. Find an expression for the current in the inductor, $i_2(t)$. 12

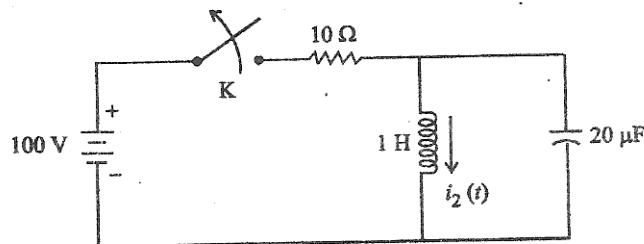


Fig. 2

Unit – II

2. (a) State and explain 'superposition theorem' and also write its limitations. 5
- (b) Determine the current in the capacitor branch by the superposition theorem, in the network of fig. 3. 15

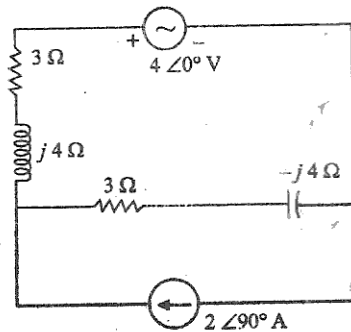


Fig. 3

Or

- (a) State and explain the following : 6
- (i) Reciprocity theorem (ii) Millman's theorem

- (b) Find the Thevenin's equivalent circuit at terminals AB for the network shown in fig. 4.

14

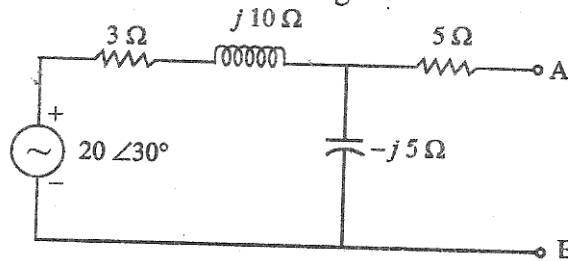


Fig. 4

Unit – III

3. (a) The waveform shown in fig. 5 occurs only once. Write an expression for $v(t)$. Find the transform $v(s)$ for $v(t)$.

8

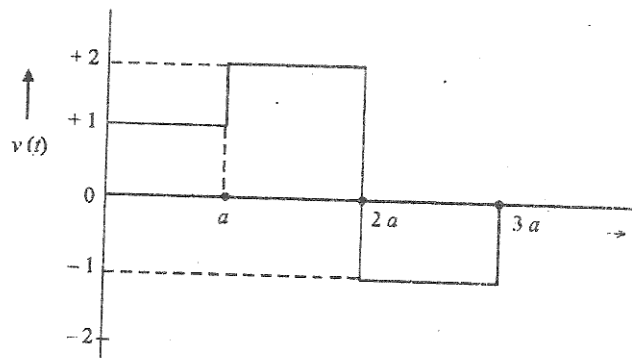


Fig. 5

- (b) A unit impulse voltage $\delta(t - 2)$ is applied to a series R-L network, where $L = 1$ H, $R = 3 \Omega$. If the impulse is applied at $t = 0$, while the initial condition of the network is $i(0) = 0$, find $i(t)$.

12

Or

- (a) Obtain the S-domain equivalent circuit for an inductor with initial current.
- (b) Define 'unit impulse function' and derive its Laplace transform.

5

5

P. T. O.

- (c) If the capacitor is uncharged and the inductor current is zero at $t = 0^-$, in the network shown in fig. 6, show that the transform of the generator current is : 10

$$I(s) = \frac{10(s^2 + s + 1)}{(s^2 + 1)(s^2 + 2s + 2)}$$

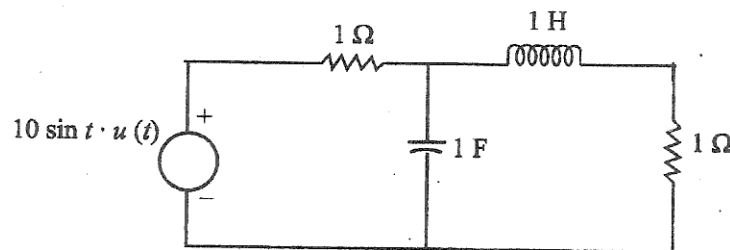


Fig. 6

Unit - IV

4. (a) What are the Dirichlet conditions for the Fourier series representation ? 4
- (b) The waveform shown in fig. 7 consists of a train of isosceles triangles. For this waveform, determine the Fourier coefficients and plot the corresponding amplitude and phase spectra. 16

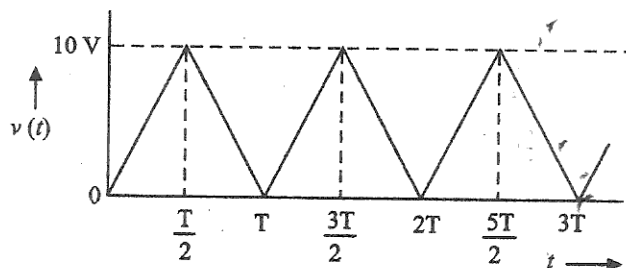


Fig. 7

Or

- (a) Explain with the help of an example the 'half-wave symmetry'. 5

- (b) Find the trigonometric Fourier series for the square wave shown in fig. 8 and plot the line spectrum. 15

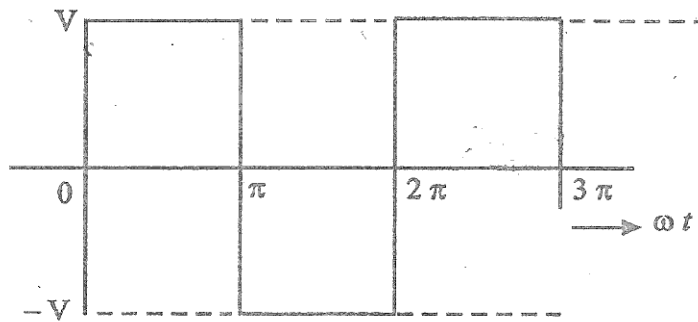


Fig. 8

Unit - V

5. (a) Define the terms 'transfer admittance' and 'voltage ratio transfer function' with reference to two-port networks. 6

- (b) Find the open circuit transfer impedance $\frac{V_2(s)}{I_1(s)}$ and open circuit voltage ratio $\frac{V_2(s)}{V_1(s)}$ for the network shown in fig. 9. 14

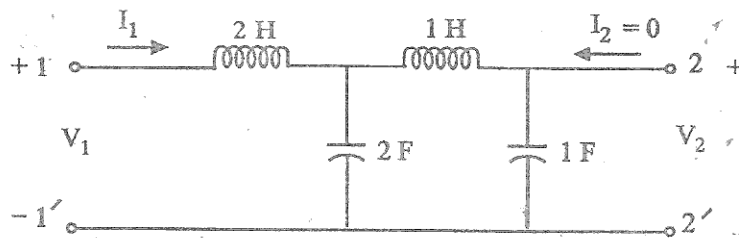


Fig. 9

Or

- (a) What are the 'open circuit impedance' parameters of two-port networks? How can the 'transmission P. T. O.

[6]

parameters' be obtained from the 'open circuit impedance' parameters ?

- (b) Find the transmission parameters (A, B, C, D) for the network shown in fig. 10.

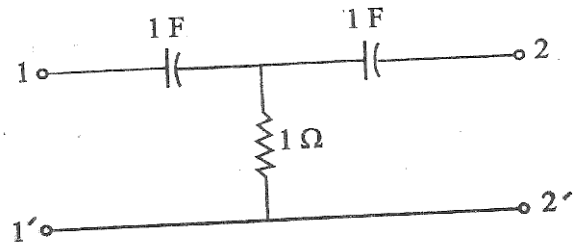


Fig. 10