BE-104

B.E. I & II Semester Examination, December 2012

Basic Electrical and Electronics Engineering (Grading System)


Time: Three Hours

Maximum Marks: 70


Note: Attempt all the questions.

Unit - I

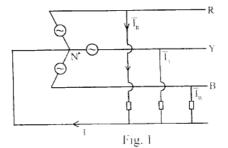A 400 volt, 3 phase 4 wire system supplies resistive loads between each of the three lines and neutral.
Calculate the lines and neutral current when the phase sequence is RYB.



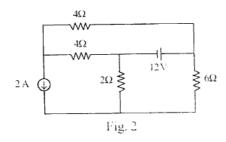- 2. a) State Thevenin's Theorem giving an example. 4
 - b) Using Thevenin's Theorem find the current flowing through 6Ω resistor of the network shown in Fig. 2.



Or

- 3. A balanced star connected load is supplied from a symmetrical 3 phase 400 volt (line to line) supply. The current in each phase is 50 Amp and lags 30° behind phase voltage. Find
 - a) Phase voltage

- b) Phase impedance
- c) Active and reactive power drawn by the load. Also draw the phasor diagram for the same. 7
- 4. Explain in brief the following:
 - a) Active and reactive power
- b) Apparent power
- c) Power factor

- d) Balanced and unbalanced supply
- e) Superposition theorem.

Unit - II

- 5. What are the assumptions made for an ideal transformer. Draw the equivalent circuit and phasor diagram of an ideal transformer.
- 6. An audio frequency transformer in employed to couple a 60Ω resistive load to a source of 6 volt in series with the resistance of 2400 Ω .

[2]

- Determine the transformer turns-ratio to ensure the maximum power is transferred to the load.
- b) Calculate the value of maximum power and corresponding load current and voltage. 7

Or

- 7. How transformer is used for impedance transformation. Explain the no load test used for the transformer parameter determination.
- State Ampere's circuit law. What is mmf and flux density. How ampere circuital law is used in magnetic circuit analysis. Explain Hysteresis and Eddy current losses.

Unit - III

- Explain the constructional and operational feature of a DC machine with the help of neat diagram.
- 10. A three phase 440 volt, 50 hp, 50 Hz induction motor delivers rated output power at 1440 rpm. Find
 - a) No. of poles of machine
 - b) Synchronous speed
- c) Slip
- d) Slip rpm
- Rotor speed w.r.t. (i) Rotor structure (ii) Stator (iii) Stator rotating minf.
- f) Rotor emf at operating speed if stator to rotor turn ratio is 1:0.5. Assume winding factor is unity.

Or

- 11. What is the basic working principle of synchronous machine.
- 12. Explain Torque-slip characteristics of a 3 phase induction motor.

Unit - IV

- 13. State Demorgan's theorem. Specify the truth table and logic diagram for full adder circuit.7
- 14. Draw the logic diagram for JK flip flop. Explain its operation.

Οr

- 15. Explain the operation of clocked RS flip flop with the help of logical diagram. Truth table, symbol and characteristic equation.
- 16. Convert the following numbers into decimal.
 - i) (1001010.0101),
- ii) (12212),
- iii) (8.3)_a

Also find the 2' complement of

- i) (110110),
- -ii) (10000),

Unit - V

- 17. Draw the VI characteristics of a Germanium Diode. Explain the same.
- 18. Why BJT's are used. Explain the working of a CB transistor.

()r

- 19. Discuss the three configuration of transistor. How do they differ from each other.
- 20. What happens to the conductivity of the semiconductor and a metal when temperature is increased. Discuss with reason.