

Roll No .....

**EC - 8012****B.E. VIII Semeste**

Examination, June 2015

**Microwave Circuits****Elective - II****Time : Three Hours****Maximum Marks : 70**

- Note:** i) Attempt any one question from each unit.  
 ii) All question carry equal marks.  
 iii) Assume suitable data if any missing.

**UNIT-I**

1. a) What is the significance of impedance matching? Explain impedance match factor in brief. 7  
 b) Explain (i) single stub matching (ii) Double stub matching. Enumerate the advantages and disadvantages of each of these methods. 7

OR

2. a) Write a detail note on Binomial transformer. 7  
 b) A typical transmission line has a resistance of  $8\Omega/Km$  impedance of  $2\text{ m}\Omega/km$ , a capacitance of  $0.002\text{ }\mu F/\mu m$  and a conductance of  $0.07\text{ }\mu S/km$ . Calculate the characteristic impedance, attenuation constant, phase constant of transmission line at a frequency of  $2\text{ kHz}$ . If a signal 82 volt is applied and the line is terminated by its characteristic impedance, calculate the power delivered to the load, if the length of line is  $500\text{ km}$ . 7

**UNIT-II**

3. a) What are the different substrates available for microwave printed circuits? Explain in detail. 7  
 b) Discuss various types of losses in microstrip lines and also define Quality factor of microstrip line. 7

EC-8012

PTO

[2]

OR

4. a) What do you understand by co-planer strip lines? 7  
 b) A lossless parallel strip line has a conducting strip width  $W$ . The substrate dielectric separating the two strips has relative dielectric constant  $\epsilon_{rd}$  of 6 and thickness  $d$  of  $4\text{ mm}$ . Calculate, width  $W$  of strip in order to have characteristic impedance of  $50\Omega$ , strip line capacitance, strip line inductance and phase velocity of the wave in parallel strip. 7

**UNIT-III**

5. a) Discuss design procedure of low noise Amplifier. 7  
 b) Explain microwave amplifier design using 'S' parameters. 7

OR

6. Explain in detail: 14  
 a) Power gains  
 b) Stability

**UNIT-IV**

7. Explain the following: 14  
 a) Gunn oscillator  
 b) Balanced mixer

OR

8. a) What do you understand by Oscillators phase noise? 7  
 b) Explain mixer analysis using Harmonic Balancing. 7

**UNIT-V**

9. a) Explain the implementation of stepped impedance low pass filter. 7  
 b) What do you understand by frequency transformation and expansion? 7

OR

10. a) Write a note on Narrowband and Wideband microwave filter. 7  
 b) Discuss image parameter method of filter design in brief. 7

\*\*\*\*\*