

Roll No .....

**EX - 702**

**B.E. VII Semester**

Examination, December 2016

**Electrical Drives**

**Time : Three Hours**

**Maximum Marks : 70**

Note: i) Answer any five questions.

ii) All questions carry equal marks.

1. a) Draw and explain the block diagram of electric drives. 7  
b) Explain the operation of single phase fully controlled converted fed separately excited D.C. motor drives. 7
2. a) Explain with circuit diagram of a single phase dual converter feeding a separately excited motor. 7  
b) A 220V, 1000 rpm, 60A separately excited d.c. motor has an armature resistance of  $0.1\Omega$ . It is fed from a single phase full converter with an a.c. source voltage of 230V, 50Hz. Assuming continuous conditions, compute. 7  
i) Firing angle for rated motor torque at 600 rpm.  
ii) Motor speed for  $\alpha = 150^\circ$  and half rated torque.
3. a) State and explain the important features of various braking methods of d.c. motors. 7  
b) Mention the drawbacks of rectifier fed d.c. drives. 7
4. a) Explain the cyclo converter fed induction drive with the help of block diagram. 7  
b) In the V/f control scheme of three phase induction motor if we vary the voltage, why we have to vary frequency? Explain. 7

5. a) Describe static Kramer drive for speed control of induction motor. 7  
b) Describe static Scherbius drive for speed control of induction motor. 7
6. a) Explain VSI fed self controlled synchronous motor drive with neat circuit diagram. 7  
b) Why the load commutated inverter fed synchronous motor drive is found suitable for high speed and high power applications. 7
7. a) Write the applications of synchronous motor? 7  
b) State and explain the roles of a damper winding in a synchronous motor. 7
8. a) Explain the speed-torque characteristics of a d.c. motors. 7  
b) Explain the speed torque characteristics of a three phase induction motor. 7

\*\*\*\*\*