

Total No. of Questions : 10 ] [ Total No. of Printed Pages : 4

Roll No. ....

## CS/IT-304(N)

B. E. (Third Semester) EXAMINATION, Dec., 2010

(New Scheme)

(Common for CS & IT Engg. Branch)

ELECTRONIC DEVICES AND CIRCUITS

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

**Note :** Attempt *one* question from each Unit. All questions carry equal marks.

### Unit-I

- (a) With the help of energy band diagram explain the principle of working of tunnel diode.
- (b) Determine the quiescent levels of  $I_{CQ}$  and  $V_{CEQ}$  for the network of fig.1.

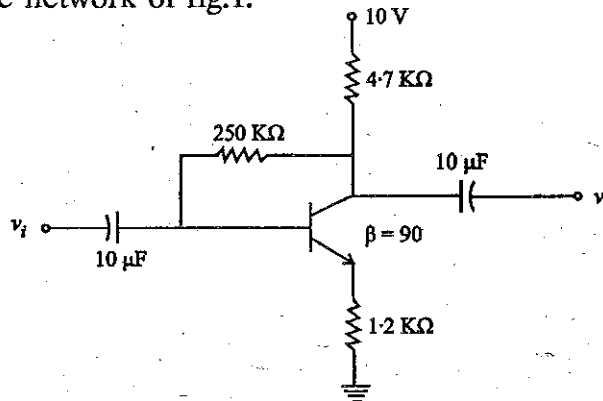


Fig. 1

P. T. O.

[ 2 ]

CS/IT-304(N)

Or

2. (a) Explain the principle of working of depletion type MOSFET.
- (b) With the help of high frequency model of a CE transistor, explain its working.

**Unit – II**

3. (a) Calculate the voltage gain of the circuit of fig. 2.

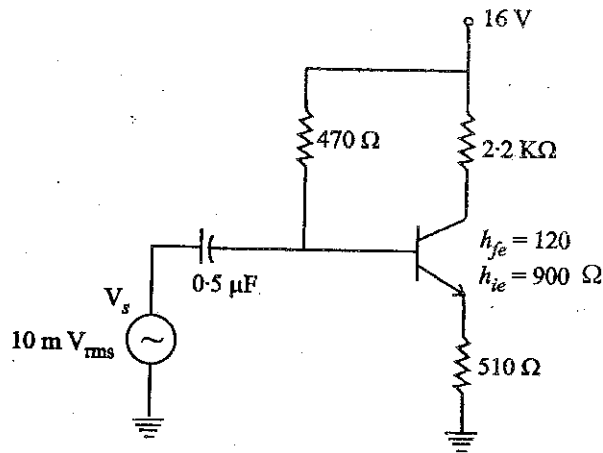


Fig. 2

- (b) Determine the efficiency of class A power amplifier.

Or

4. (a) Explain the principle of working of RC phase shift oscillator.
- (b) Determine the gain and input-output impedance of voltage series feedback amplifier.

**Unit – III**

5. (a) With the help of timing diagram explain the working of Astable multivibrator.
- (b) Calculate the differential mode gain, common mode gain and CMRR using  $h$ -parameters.

[ 3 ]

CS/IT-304(N)

Or

6. (a) Obtain the output waveform of the circuits shown in fig. 3.

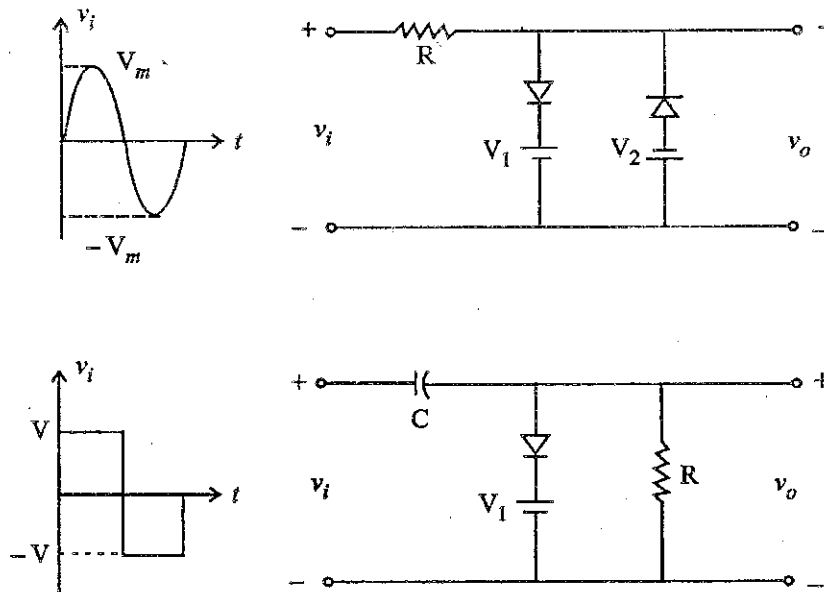


Fig. 3

- (b) Explain briefly cascade and cascode amplifiers.

#### Unit – IV

7. Explain the following application of op-amp. :

- Summer
- Integrator
- Log amplifier
- Voltage to current converter

Or

- (a) With the help of circuit diagram explain the working of op-amp. as comparator.
- (b) Explain briefly about active filters and its types.

P. T. O.

[ 4 ]

Unit – V

9. (a) Explain the working of series regulator.  
(b) Explain the current limiting circuits.

*Or*

10. Write short notes on the following :
  - (a) Fixed switching regulator
  - (b) UPS