

Roll No

CS-3003 (CBGS)**B.E., III Semester**

Examination, May 2018

Choice Based Grading System (CBGS)**Digital Circuit and Design***Time : Three Hours**Maximum Marks : 70*

- Note:** i) Attempt any five questions.
ii) All questions carry equal marks.

1. a) Convert $(41.6875)_{10}$ to 7
 - i) Binary
 - ii) Octal
 - iii) Hexadecimal
- b) Justify the following statements with examples. 7
 - i) Excess-3 code is self complementary code
 - ii) Gray code is a reflected code
2. a) Write five theorem of Boolean Algebra and simplify 7
 $F = (A+B)'(A'+B)'$
- b) Realize NAND, NOR and NOT gates using transistors. 7
3. Simplify the Boolean function with don't care conditions and implement it with NAND gates 14
 $F(wxyz) = \Sigma (1, 3, 7, 11, 15)$
 $d(wxyz) = \Sigma (0, 2, 5)$

4. a) How to design a combination circuit? Design a Full Adder circuit. 7
- b) Draw and explain the working of monostable multivibrator. 7
5. a) Define Fan-out and Figure of merit. Compare TTL, ECL and CMOS logic families. 7
- b) What is Decoder? Explain how combinational circuits like full adder can be implemented with decoder. 7
6. a) Design a BCD to excess-3 code converter. 7
- b) Design a MOD-5 counter. 7
7. a) Explain any one type of Analog to digital converter in detail. 7
- b) What is shift register? Draw and explain shift left-right register. 7
8. Write a short notes on (any two): 14
 - a) PLA
 - b) Multiplexer
 - c) V-F converter
 - d) Encoder
