

Total No. of Questions : 10 ] [ Total No. of Printed Pages : 3

Roll No. ....

**BE-104**

**B. E. (First Semester) EXAMINATION, Dec., 2010**

(Grading System)

(Common for all Branches)

**BASIC ELECTRICALS AND ELECTRONICS  
ENGINEERING**


*Time : Three Hours*

*Maximum Marks : 70*

*Minimum Pass Marks : 22 (D Grade)*

**Note :** Attempt any *five* questions. All questions carry equal marks.

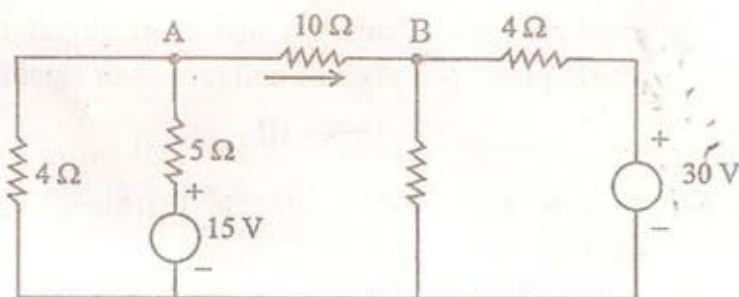1. (a) Explain ideal voltage source and ideal current source with neat diagrams. How ideal voltage source can be converted into ideal current source ?
- (b) Using nodal analysis, find the current through the  $10\ \Omega$  resistor in the figure shown below.



P. T. O.

Or

2. (a) State and explain superposition theorem with the help of an example.
- (b) Establish the relationship between phase and line voltages in a 3-phase star connected circuit.

### Unit—II

3. (a) Discuss in brief about the construction and basic principle of operation of transformer.
- (b) Draw and explain the phasor diagram of a single phase transformer under lagging load condition.

Or

4. (a) The following readings were obtained for O.C. and S.C. tests on 8 kVA, 400/120 V, 50 Hz transformer :

O.C. test (L.V. side) : 120 V, 4 A, 75 W

S.C. test (L.V. side) : 9.5 V, 20 A, 110 W

Find :

- (i) The equivalent circuit parameters referred to H.V. side.
- (ii) Efficiency at half load and 0.8 P. F. lagging
- (b) Explain open circuit test and short circuit test of a single phase transformer and give their significance.

### Unit—III

5. (a) Classify the rotating electric machines with their applications.
- (b) Explain the concept of rotating magnetic field in a 3-phase induction motor.

Or

6. (a) An 8-pole wave connected D.C. generator has 900 armature conductors and flux per pole of 0.04 Wb. At what speed it must be driven to generate 500 V ?
- (b) Explain the working principle and construction of D.C. machine.

## Unit-IV

7. (a) What is octal number system ? How will you convert :
- An octal number into decimal number
  - Decimal number into octal number ?
- Explain with an example.
- (b) Using 2's complement subtract  $(100111)_2$  from  $(110011)_2$ .

Or

8. (a) Define NAND and NOR gate and give their truth tables.
- (b) What is a Half Adder ? How is it realised using logic gates ?

## Unit-V

9. (a) What do you understand by intrinsic and extrinsic semi-conductors ?
- (b) Discuss the behaviour of P-N junction diode under forward and reverse biasing.

Or

10. (a) Draw the circuit of various transistor configurations. List their important features.
- (b) What do you understand by transistor biasing ? Give its importance.