

Roll No

EX-504 (GS)**B.E. V Semester**

Examination, December 2017

Grading System (GS)**Power Electronics Devices and Circuits***Time : Three Hours**Maximum Marks : 70*

- Note:** i) Attempt any five questions.
ii) All questions carry equal marks.

1. a) Explain working of GTO with VI characteristics. 7
b) Describe the different types of protection schemes for SCR. 7
2. a) Discuss the effect of source inductance on operation of single phase fully controlled rectifier. 7
b) Draw the waveform of 3-phase controlled rectifier on RL load at 60° firing angle. 7
3. a) What are the difference between voltage source and current source inverter? Explain. 7
b) Explain operation of 3-phase bridge inverter with 120° mode of operation. 7
4. a) Explain the various control strategies used for chopper circuits. 7
b) Describe the working of class C chopper with neat and clean waveform. 7

EX-504 (GS)

130

PTO

5. a) Explain the single phase dual converter with proper diagram and different waveform. 7
b) What kind of controller required for control of FAN? Explain with circuit diagram and waveform. 7
6. a) Discuss effect of free wheeling diode on the performance of $1-\phi$ rectifiers. 7
b) Explain UJT firing circuit for SCR with proper circuit diagram and waveform. 7
7. a) Explain two transistor analogy of SCR. Also describe the VI characteristics of SCR. 7
b) What kind of switch required to design rectifier and why? Draw the symbol of 6 power electronics switches. 7
8. Write short notes on any two of the following: 14
a) Buck-Boost chopper
b) Harmonics elimination technique in inverter
c) Class B Commutation

EX-504 (GS)

131