

Total No. of Questions : 10 ] [ Total No. of Printed Pages : 4

Roll No. ....

## BE-104

B. E. (First/Second Semester)

EXAMINATION, June, 2010

(Common for all Branches)

BASIC ELECTRICAL ENGINEERING

(BE – 104)

Time : Three Hours

Maximum Marks : 100

Minimum Pass Marks : 35

**Note :** Attempt only five questions. One question from each Unit is to be attempted worth 20 marks only.

### Unit – I

1. (a) Distinguish between the following : 6
- (i) Active and Passive elements
  - (ii) Node and Junction
  - (iii) Loop and Mesh
- (b) Find the current through 4 ohm resistor using node equation method in fig. 1. 14

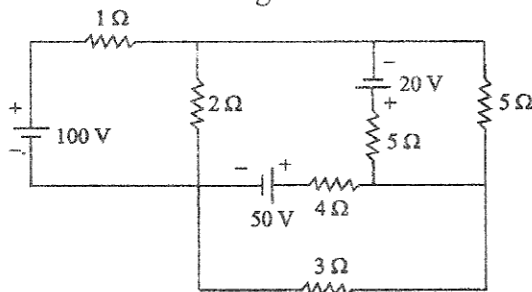


Fig. 1

P. T. O.

Or

2. While applying Kirchhoff's voltage law to a loop how signs are applied to the emf and voltage drops ?

Apply Kirchhoff's law in the circuit shown in fig. 2, determine the value  $E_2$  which will reduce galvanometer current to zero. The galvanometer resistance is 10 ohm.

20

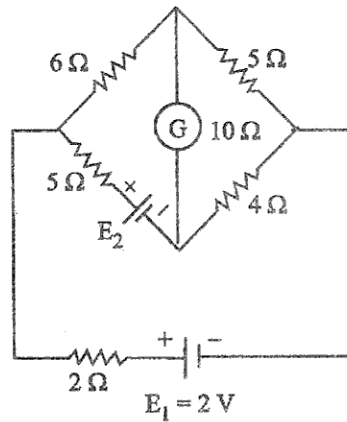


Fig. 2

### Unit – II

3. (a) Determine phase angle relationship between alternating voltage and current in a purely inductive and purely capacitive circuit under steady state condition. 10
- (b) A series R-L-C circuit consists of 100 ohm resistor, an inductor of 0.318 henry, and a capacitor of unknown value, when the circuit is energised by  $230 \angle 0^\circ$  volt, 50 Hz sinusoidal supply, the current was found to be  $2.3 \angle 0^\circ$  amperes. Find the value of capacitor in microfarad, the voltage across the inductor, the total power consumed. 10

Or

4. (a) Three-phase system is preferred over single-phase system, why ? Develop the relationship between line voltage and line current with phase voltage and phase current in star-connected and delta-connected circuits. 12
- (b) The power input to a 2000 volt, 50 Hz, 3-phase motor running on full load at an efficiency of 90% is measured by two wattmeters which indicate 300 kW and 100 kW respectively. Calculate input power, power factor, line current and HP output. 8

Unit – III

5. Define the terms mmf, magnetic flux and magnetic reluctance and establish the relation which holds between these quantities for magnetic circuit.
- Estimate the number of ampere turns necessary to produce a flux of 100000 lines round an iron ring of  $6 \text{ cm}^2$  cross-section and 20 cm mean diameter having an air gap 2 mm wide across it. Permeability of the iron may be taken 1200. Neglect the leakage flux outside the 2 mm air gap. 20

Or

6. (a) Derive an expression for field strength at the centre of a long solenoid of  $N$ -turns having a length of  $l$  metres and carrying a current  $I$  amperes. 10
- (b) Find the eddy current loss in a 50 Hz transformer core with a maximum flux density of  $1.2 \text{ Wb/m}^2$ . The core of section  $8 \text{ cm} \times 8 \text{ cm}$  and total effective length 60 cm is constructed of lamination of thickness 0.3 mm. Assume the space factor to be 0.9 and the eddy current coefficient  $6.58 \times 10^6$ . 10

[ 4 ]

**Unit-IV**

7. (a) With the help of a neat diagram explain the construction and working principle of a transformer. Also explain the function of conservator and silica gel breather. 10
- (b) Draw the equivalent circuit of a transformer and explain how the secondary parameters are transferred to primary. 10

*Or*

8. (a) Explain the following with respect to transformer : 10
- (i) Core type and shell type transformer
  - (ii) Hysteresis and eddy current loss and how they are minimised.
- (b) Draw the phasor diagram of a transformer under : 10
- (i) Resistive
  - (ii) Inductive
  - (iii) Capacitive load

**Unit-V**

9. (a) Explain with the help of a diagram the construction of a D.C. machine. 10
- (b) Derive the emf equation of a D.C. generator. 10
- Or*
10. (a) Explain the difference between 3-phase and single-phase induction motor. Also explain how single phase induction motor is started. 10
- (b) Explain how rotational field is produced in a 3-phase induction motor. 10

**BE-104**

**47,070**