

Roll No .....

**CS/EI/IC - 303****B.E. III Semester**

Examination, June 2016

**Digital Circuit and System****Time : Three Hours****Maximum Marks : 70**

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.  
 ii) All parts of each question are to be attempted at one place.  
 iii) All questions carry equal marks, out of which part A and B (Max.50 words) carry 2 marks, part C (Max.100 words) carry 3 marks, part D (Max.400 words) carry 7 marks.  
 iv) Except numericals, Derivation, Design and Drawing etc.

**Unit - I**

- Obtain excess-3 code for  $(428)_{10}$ .
  - Perform  $(52)_{10} - (89)_{10}$  using 9's complement.
  - Convert  $(43)_8 = (?)_{10} = (?)_2$
  - Minimize the following Boolean expression using Karnaugh map method.  $Y = \sum_m(1, 3, 5, 9, 11, 13)$

OR

Explain concept of Prime implicant.

**Unit - II**

- Design half adder using NAND gates.
  - Explain types of BCD adders.
  - Design full subtractor using half subtractor.
  - Discuss the working of look ahead carry generator.

OR

Design a full subtractor using minimum logic gates. Also design the circuit using all NAND gates.

**Unit - III**

- Define Bistable, Monostable and Astable multivibrator.
  - Describe the application of monostable multivibrator.
  - Draw basic diagram of Schmitt trigger and explain it.
  - Design a NAND gate, using CMOS logic and explain its working.

OR

How is interfacing TTL to MOS obtained?

**Unit - IV**

- How many flip flops are required to construct a MOD-128 counter? What is the largest decimal number that can be stored in a mod-64 counter?
  - What modules counters can be constructed with the use of four flip-flops? **www.rgpvonline.com**
  - Explain synchronous and asynchronous counters.
  - Design a 4-bit Johnson counter.

OR

Design a BCD to gray code converter.

**Unit - V**

- Explain sample and hold circuit.
  - Describe V-F convertor.
  - Write short notes on 2-bit simultaneous A/D converter.
  - Explain with the help of block diagram any one type of analog to digital converter.

OR

With the help of block diagram explain one type of digital to analog converter.