

Total No. of Questions : 8]

[Total No. of Printed Pages : 2

Roll No

EE/EX-4003 (CBGS)**B.E. IV Semester**

Examination, May 2018

Choice Based Grading System (CBGS)**Digital Electronics Logic Design****Time : Three Hours****Maximum Marks : 70**

- Note:** i) Attempt any five questions.
ii) All questions carry equal marks.

1. a) Convert the following:
 - i) $(0.828125)_{10} = (?)_2$
 - ii) $(18.6)_9 = (?)_{11}$
 - iii) $(234)_{10} = (?)_8$
 - iv) $(AF.16C)_{16} = (?)_8$
 - v) $(4163)_{10} + (7520)_8 = (?)_2$
- b) Explain error detecting and correcting codes with examples.
2. a) Implement $f(x, y, z) = \sum m(0, 3, 4, 5, 7)$ in NAND logic.
- b) Design a 32101 multiplexer using 8 to 1 multiplexers having an active LOW ENABLE input and a 2-to-4 decoder.
3. a) Explain how to convert serial data to parallel and parallel data to serial using shift registers.
- b) Realize D and T flip flops using JK flip flops.

[2]

4. a) Design a 3-bit synchronous up/down modulo 5 counter.
- b) With neat sketch, explain the operation of a 3-bit universal shift register.
5. a) What is memory expansion? Explain.
- b) Design a 3×8 decoder and implement it using a suitable PLA.
6. a) Design a magnitude comparator to compare two 3-bit numbers:
 $A = A_2 A_1 A_0$ and $B = B_2 B_1 B_0$
- b) Design a 3×3 Binary (array) multiplier.
7. a) State and prove De-morgan's theorem.
- b) Minimize the following function using K-map:
 $f(A, B, C, D, E) = \sum m(1, 3, 5, 8, 9, 11, 15) + d(2, 13)$
8. Write short notes on any two :
 - a) PLA
 - b) Synchronous MOD-6 counter
 - c) FPGA
