

Roll No

CS/IT-304**B.E. III Semester**

Examination, June 2016

Electronics Devices and Circuit**Time : Three Hours****Maximum Marks : 70**

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
 ii) All parts of each question are to be attempted at one place.
 iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks.
 iv) Except numericals, Derivation, Design and Drawing etc.

Unit-I

1. a) What is dynamic resistance of FET?
- b) Define pinch-off voltage of FET.
- c) Write a note on MOSFET.
- d) Explain the operation of a N channel MOSFET with the help of its characteristics.

OR

Define α and β of a transistor and derive relationship between them.

Unit-II

2. a) Write a note on voltage gain of amplifier.
- b) Write a short note on power amplifier.
- c) How do positive and negative feedback in amplifier differ from each other? Explain.
- d) Show that the maximum conversion efficiency of class B amplifier is 78.5%.

OR

Explain the working principle of Wien's bridge oscillator circuit.

Unit-III

3. a) Write a note on multivibrator.
- b) What do you mean by a clamper?
- c) Write a note on bistable multivibrator.
- d) Explain the operation of a positive clipper with suitable waveforms.

OR

Explain the transfer characteristic of differential amplifier.

Unit-IV

4. a) Write a note on closed loop gain of an Op-Amp.
- b) Explain significance of slew rate of an Op-Amp.
- c) Explain the offset voltage and offset current of an Op-Amp.
- d) Explain log and antilog amplifier circuit using Op-Amp.

OR

Explain the integrator using Op-Amp with circuit diagram.

Unit-V

5. a) Write a note on Voltage Regulator.
- b) What is meant by Load Regulation of a power supply?
- c) Explain in brief the working of a series regulated power supply.
- d) With block diagram explain the working of SMPS.

OR

With block diagram explain three terminal IC voltage regulator.
