

Total No. of Questions : 10 ] [ Total No. of Printed Pages : 3

Roll No. ....

## EC-403(N)

**B. E. (Fourth Semester) EXAMINATION, June, 2010**

(New Scheme)

(Electronics & Communication Engg. Branch)

DIGITAL ELECTRONICS

[EC-403(N)]

*Time : Three Hours*

*Maximum Marks : 100*

*Minimum Pass Marks : 35*

**Note :** Attempt *one* question from each Unit. All questions carry equal marks.

### Unit-I

1. (a) Convert the following :

(i)  $(329.54)_{10} = ( )_{16}$

(ii)  $(BD02.1A)_{16} = ( )_{10}$

(iii)  $(1101)_{\text{gray}} = ( )_2$

(iv)  $(967.345)_{10} = ( )_8$

(v)  $(BA05.49A)_{16} = ( )_4$

(b) Minimise the following function using K-map and then realise it using NOR gate :

$$Y = \overline{AB} \cdot \overline{CD} \cdot AD$$

P. T. O.

Or

2. (a) Simplify the following expression using Boolean algebra :

(i)  $\overline{A \overline{B} + ABC + A(B + A \overline{B})}$

(ii)  $(A + B)(\overline{A} \overline{C} + C)(\overline{B} + AC)$

- (b) Find the minimal sum of products for the Boolean expression  $f = \Sigma (1, 2, 3, 7, 8, 9, 10, 11, 14, 15)$ , using the Quine-McCluskey method.

#### Unit – II

3. (a) Design a 4 bit parallel Adder/Subtractor.  
(b) Explain the working of a look ahead carry generator.

Or

4. (a) Implement the following function using a multiplexer :  
 $F(A, B, C, D) = \Sigma (1, 5, 6, 7, 8)$   
(b) Design a BCD to Binary code converter.

#### Unit – III

5. (a) With the help of circuit diagram and timing diagram explain the working of Astable Multivibrator.  
(b) Explain the working of JK flip-flop. What is the need of triggering in the flip-flops and how it is achieved ?

Or

6. Design a MOD-11 ripple counter using J-K flip-flop.

#### Unit – IV

7. (a) Design a combinational circuit that gives a binary output equal to the square of binary coded decimal number 0 through 9 using diode matrix ROM.

[ 3 ]

- (b) Explain the working of Bipolar PROM array with fusible links.

*Or*

8. (a) Explain the architecture and working of field programmable gate array.  
(b) Design a binary to excess-3 code converter using PLA.

**Unit – V**

9. (a) Discuss the major difference between a bipolar integrated circuit and a MOS integrated circuit.  
(b) Explain ECL logic. Why is it faster than TTL logic ?

*Or*

10. (a) Explain the working of CMOS logic. Justify that its switching speed is greater than PMOS/NMOS.  
(b) What are BiCMOS logic circuits ? What are their advantages ?