

**404**

**B. E. (Fourth Semester) EXAMINATION, June, 2009**

**(New Scheme)**

**(Common for EC, EI & BM Engg.)**

**ELECTRONIC CIRCUITS**

*Time : Three Hours*

*Maximum Marks : 100*

*Minimum Pass Marks : 35*

**Note :** Attempt *one* question from each Unit. All questions carry equal marks.

**Unit – I**

1. (a) The BJT of fig. 1, given below has the parameter :


$$h_{ie} = 2000 \text{ ohms}$$

$$h_{fe} = 100$$

$$h_{re} = 5 \times 10^{-4}$$

$$h_{oe} = 2.5 \times 10^{-5} \text{ mhos}$$

Find the voltage gain and A. C. input impedance.

 

**Fig. 1**

- (b) Discuss voltage divider biasing (self bias) technique for BJT. Also give its merits and demerits.

Or

2. (a) Give low frequency  $h$ -parameter model of BJT and derive expressions for voltage and current gain for CE configuration.
- (b) Calculate the value of collector current and collector-to-emitter voltage for the d. c. bias circuit shown in fig. 2.

 


Fig. 2

Also draw the load line and locate Q-point on it. Assume  $V_{BE} = 0.7$  V.

3. (a) Discuss the principle of Negative Feedback in amplifier with a neat diagram. Derive an expression for the gain and bandwidth.
- (b) An amplifier has a mid-frequency gain of 100 and a bandwidth of 200 kHz.
- What will be the new bandwidth and gain, if 5% negative feedback is introduced ?
  - What should be amount of feedback, if the bandwidth is to be restricted to 1 MHz ?

Or

4. (a) Sketch circuit of a Wien's bridge oscillator. Explain its working. Determine frequency of oscillation. Will oscillation take place, if bridge is balanced ? Explain.
- (b) Design a phase shift oscillator to operate at a frequency of 2 kHz using a JFET. Assume that  $\mu = 50$ ,  $A_v = 40$  and  $r_d = 5 \text{ K } \Omega$  and the phase shift network does not load the amplifier.
- (i) Find the minimum value of  $R_D$  to be used in the drain circuit.
- (ii) Find the value of the RC product.
- (iii) Chose reasonable values of R and C to make this oscillator work satisfactory.
5. (a) Show that the maximum conversion efficiency of an idealized Class-B amplifier (push pull configuration) is 78.5%.
- (b) Draw the circuit of a push-pull amplifier stage using two transistors and explain its working.

Or

6. (a) What is meant by term cross-over distortion ? How it is reduced ?
- (b) Explain the following terms for series resonance circuit :
- (i) Q-factor
- (ii) Selectivity and Bandwidth
7. (a) Draw the circuit diagram of Darlington's amplifier. Explain it.
- (b) Write a short note on R. C. coupled amplifier.

*Or*

8. (a) Write short notes on the following :
- (i) CMRR
  - (ii) Slew rate
  - (iii) Input offset voltage
- (b) Draw bootstrapped Darlington's circuit and explain how this increases the input resistance.
9. (a) Draw and explain the working of comparator using op-amp.
- (b) Write short note on any *one* of the following :
- (i) Logarithmic amplifier
  - (ii) Current-to-voltage converter

*Or*

10. (a) Sketch the circuit of an Integrator op-amp. and derive the expression for the output voltage, giving its applications.
- (b) Draw the circuit diagram of Schmitt trigger using op-amp. and explain its working in detail.