

EC-226**B.E. IV Semester**


Examination, June 2017

Choice Based Credit System (CBCS)**Integrated Circuits and its Application****Time : Three Hours****Maximum Marks : 60**

- Note:** i) Attempt any five questions.
ii) All questions carry equal marks.

- What are the Advantages and Disadvantages of negative feedback?
 - Derive the relevant expression to prove that input resistance increases and output resistance decreases in case of voltage series feedback.
- What is Barkhausen criteria? Explain how oscillations start in an oscillator.
 - Explain the construction and working of RC phase shift oscillator.
- Find the frequency of the oscillations of a Colpitts oscillator having $C_1 = 150\text{pF}$, $C_2 = 1.5\text{nF}$ and $L = 50\text{H}$.
 - Explain with the help of a circuit diagram, the working of an RC phase shift oscillator.
- Draw the block diagram of an op-amp and write the function of each block.

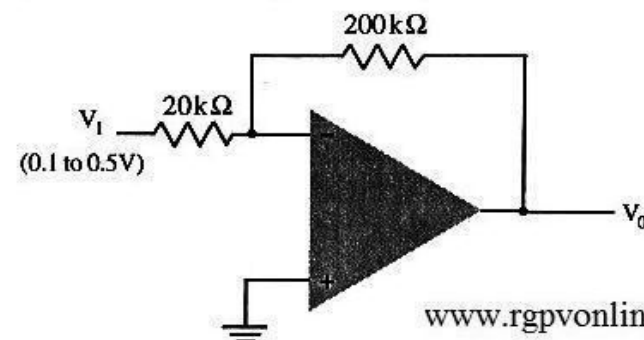- b) What is the range of the output voltage in the circuit of figure below if the input can vary from 0.1 to 0.5V?



- Assuming slew rate for 741 is $0.5\text{V}/\mu\text{sec}$. What is the maximum frequency of undistorted sine wave that can be obtained for
 - 12V peak
 - 2V peak
 - Define the following:
 - CMRR
 - PSRR
 - Input offset current
 - Output voltage swing
- It is desired to get an output using op-amp, given by the equation $V_o = 5(V_1 - V_2) + 3V_3$. Design the circuit and draw the designed circuit.
 - Draw and explain zero crossing detector with I/p and O/p waveform.
- Design a low pass filter with a cut off frequency of 1kHz and with a pass band gain of 2.
 - Draw the circuit of a first order Butterworth low pass filter and derive its transfer function.
- Write short notes on any two:
 - Active peak detector
 - Op-Amp based Wein Bridge oscillator
 - Voltage controlled oscillator