

Total No. of Questions :8]

[Total No. of Printed Pages :2

Roll No.

MEPE-102**M.E/M.Tech. I Semester**

Examination, June 2017

Power Electronics Devices and Phase Control*Time : Three Hours**Maximum Marks : 70*

- Note: i) Answer any five questions.
ii) All questions carry equal marks.

www.rgpvonline.com

1. a) List the different members of the thyristor family. Draw their characteristics and explain in brief.
b) Compare SCR, power BJT, MOSFET and IGBT on the basis of following parameters:
i) Operating frequency ii) Trigger circuit
iii) Drop iv) Snubbers
v) V-I rating vi) Applications
2. a) Explain the basic requirements for the successful firing of thyristor.
b) What are the different methods for turning off a silicon controlled rectifier and explain in brief with a neat circuit diagram.
3. a) Explain the sequence and sector control method for controlling the output voltage of phase controlled circuits.
b) Describe a procedure for designing of chopper circuit.
4. a) What are the harmonics reduction techniques? Explain multiple pulse control technique to mitigate harmonics.
b) Explain the principle of step-up chopper and multiphase chopper with output waveforms.

www.rgpvonline.com

368

MEPE-102

PTO

[2]

5. a) Discuss the single phase dual converter under circulating current conduction mode of operation and derive the expression for inductor voltage.
b) Describe the operation of multistage sequence control of ac voltage controllers with neat diagram.
6. a) Explain the operation of single phase to single phase step down cyclo converter with voltage and current waveforms for
i) Continuous load current www.rgpvonline.com
ii) Discontinuous load current
b) Describe symmetrical and asymmetrical control methods to control the output of cycloconverter.
7. a) Differentiate between the working of voltage source and current source inverters. Explain the working of 1- ϕ full bridge inverter and draw the waveshapes of output-current when:
i) Load is pure resistive
ii) Load is pure inductive
iii) Load is R-L-C under damped
b) The 1- ϕ quasi-square wave bridge inverter operates from DC supply of 200 V at a frequency of 100 Hz and feeds a resistive load of 10 Ω . Calculate
i) Duration of ON period if the rms value of the load voltage is 100 V
ii) Peak supply current
iii) Average (DC) supply current
8. Write a short note on any two of the following:
i) Protection circuits www.rgpvonline.com
ii) Design of rectifier circuit
iii) Regenerative braking using phase controlled circuits
iv) Converter reactions on load side

***** 369

MEPE-102