

Write short notes on the following :

- i) PLL
- ii) Fixed and adjustable voltage regulator
- iii) Frequency shift keying

\*\*\*\*\*

Roll No .....

**EC/EI/IC-404 (New)**

**B.E. IV Semester**

Examination, December 2016

**Linear Integrated Circuits and Its Applications**

*Time : Three Hours*

*Maximum Marks : 70*

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
- ii) All parts of each question are to be attempted at one place.
- iii) All questions carry equal marks, out of which part A and B (Max.50 words) carry 2 marks, part C (Max.100 words) carry 3 marks, part D (Max.400 words) carry 7 marks.
- iv) Except numericals, Derivation, Design and Drawing etc.

**Unit - I**

1. a) Draw the block diagram of an Op-Amp and explain it.
- b) Write down the various types and applications of Op-Amp.
- c) Draw the virtual ground of Op-Amp and write down the characteristics of an ideal Op-Amp.
- d) Draw and discuss the inverting and non inverting Op-Amp configurations.

OR

Draw the equivalent circuit of an Op-Amp and write down the expressions for input resistance, voltage gain, collector current and output voltage.

**Unit - II**

2. a) Discuss input offset voltage, Input offset current of an Op-Amp.  
b) Discuss input bias current, differential input resistance and input voltage range of Op-Amp.  
c) Discuss common mode rejection ratio and large signal voltage gain of Op-Amp.  
d) Write short notes on the following :  
i) Slew rate  
ii) Op-Amp open loop configurations  
iii) Voltage transfer curve of Op-Amp

OR

Write short notes on the following :

- i) PSRR and gain bandwidth product  
ii) Interpretation of TL082 data sheet

**Unit - III**

3. a) Discuss the characteristics of positive and negative feedback circuits.  
b) Draw the block diagram of current to voltage converter and show that it is a special case of an inverting amplifier.  
c) Draw the circuit of a summing amplifier and integrators and explain it.  
d) Calculate the voltage gain the input resistance, the output resistance and the bandwidth for a differential amplifier configuration.

OR

Write short notes on the following :

- i) Wien bridge oscillator  
ii) Voltage series and voltage shunt feedback amplifier

**Unit - IV**

4. a) Give the classification and characteristics of filters.  
b) Discuss low pass filters giving suitable diagram.  
c) Write a short note on notch filter.  
d) Discuss Chebyshev filter and its characteristics giving suitable expressions.

OR

Write short notes on the following :

- i) Butterworth 1<sup>st</sup> order high pass filter  
ii) All pass filter and self tuned filters

**Unit - V**

5. a) Write short notes on comparator.  
b) Clipper and clamper circuits.  
c) Discuss zero crossing detector giving suitable diagram.  
d) Draw and discuss monostable multivibrator giving suitable expressions and wave forms.

OR