

OR

10. a) What is a reciprocal network? Derive the condition for reciprocity in terms of 'z' parameters.
- b) The network shown in Fig. 10 contains a current-controlled current source. For this network find the 'Y' parameters.

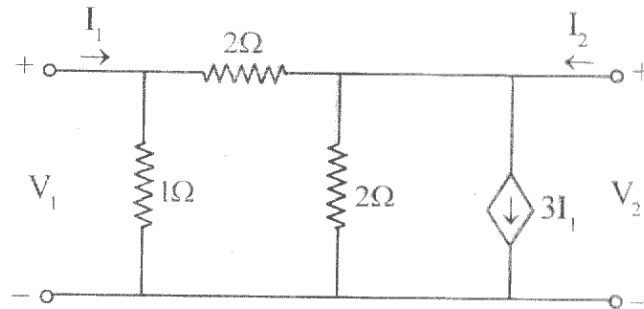


Fig. 10

RGPVONLINE.COM

Roll No

EC - 305**B.E. III Semester**

Examination, December 2013

Network Analysis*Time : Three Hours*

RGPVONLINE.COM

Maximum Marks : 70

- Note:** 1. Attempt *five* questions, selecting one question from each unit.
2. All questions carry equal marks.

Unit - I

1. a) Discuss the properties of an ideal current-source and an ideal voltage source. Explain how a voltage source can be converted into an equivalent current source and vice versa.
- b) Draw the dual of the network shown in Fig. 1.

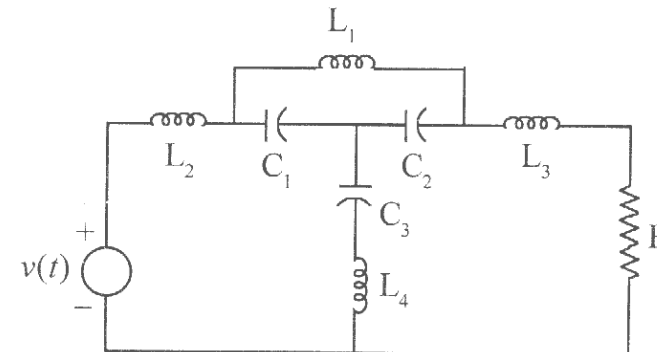


Fig. 1

OR

2. a) Explain series and parallel resonance. What are their similarities and dissimilarities?
- b) Following data refers to two coupled coils 1 and 2, as shown in Fig. 2.
- $\phi_{11} = 0.5 \times 10^{-3} \text{ Wb}$; $\phi_{12} = 0.3 \times 10^{-3} \text{ Wb}$; $N_1 = 100$ turns;
 $N_2 = 500$ turns; $i_1 = 1 \text{ A}$.
- Find, K , the coefficient of coupling, the inductances L_1 and L_2 and M , the mutual inductance.

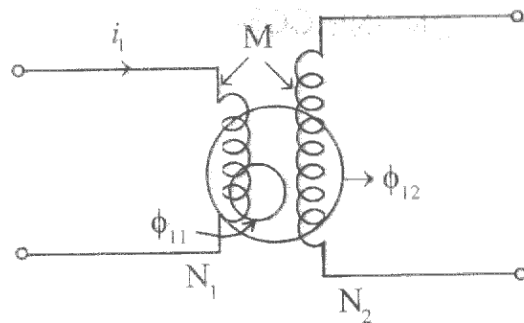


Fig. 2

Unit - II

3. a) For the network shown in Fig. 3, draw the graph and write down the tie-set matrix.

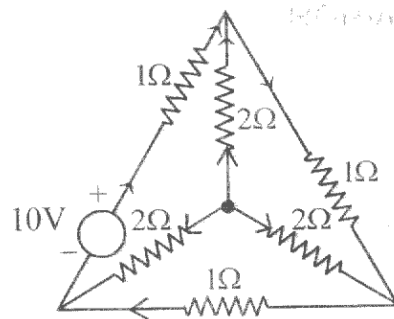


Fig. 3

- b) State and explain the following
- Reciprocity theorem
 - Millman's theorem

[3]

OR

4. State and explain 'Maximum power transfer theorem'.
 In the network shown in Fig. 4, determine Z_L so that the power absorbed by it is maximum and the value of the power absorbed.

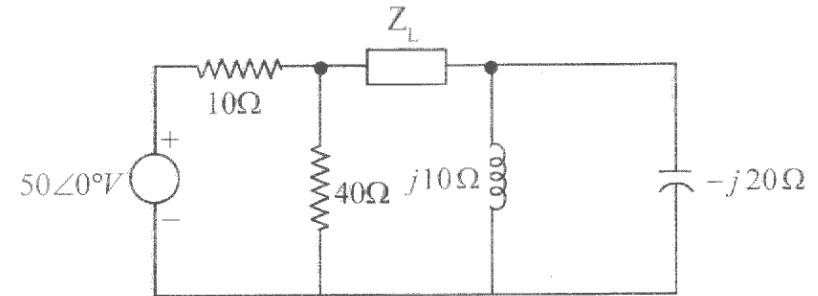


Fig. 4

Unit - III

5. In the network shown in Fig. 5, the voltage source follows the law $v(t) = Ve^{-\alpha t}$, where α is a constant. The switch is closed at $t = 0$.

- a) Solve for the current assuming that $\alpha \neq \frac{R}{L}$
- b) Solve for the current when $\alpha = \frac{R}{L}$.

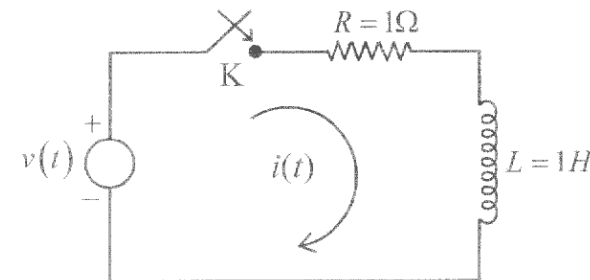


Fig. 5

OR

6. a) Discuss the initial conditions in a network. Outline the procedure for evaluating the initial conditions in network problems.
- b) In the network shown in Fig. 6, the switch K is closed at $t = 0$, with zero capacitor voltage and zero inductor current.

Solve for

- i) v_1 and v_2 at $t = 0_+$ ii) v_1 and v_2 at $t = \infty$
- iii) $\frac{dv_1}{dt}$ and $\frac{dv_2}{dt}$ at $t = 0_+$

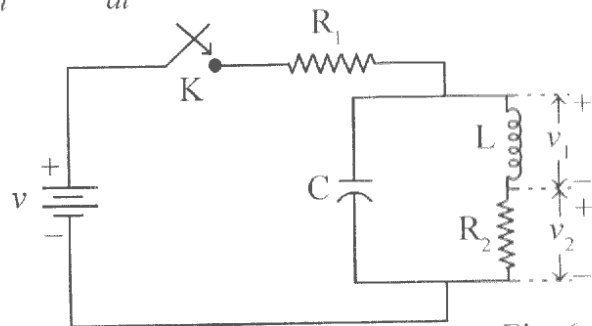


Fig. 6

RGPVONLINE.COM

Unit - IV

7. a) Define 'Unit impulse function' and derive its Laplace transform.
- b) In the network shown in Fig. 7, the switch is in position 'a' until a steady state is reached. At $t = 0$, the switch is moved to position 'b'. Under that condition, determine the transform of the voltage across the $\frac{1}{2}F$ capacitor using Thevenin's theorem.

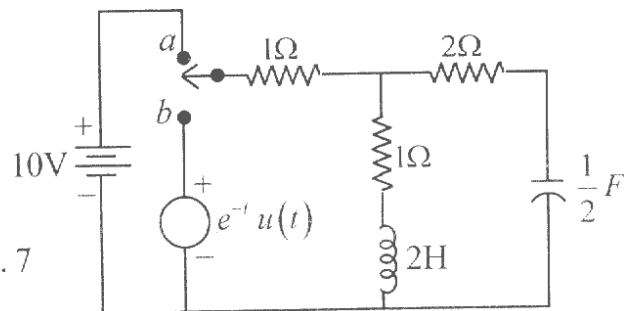


Fig. 7

OR

8. a) Discuss the effect of symmetry for a periodic function to determine the trigonometric Fourier series coefficients.
- b) Find the Fourier coefficients for the waveform shown in Fig. 8.

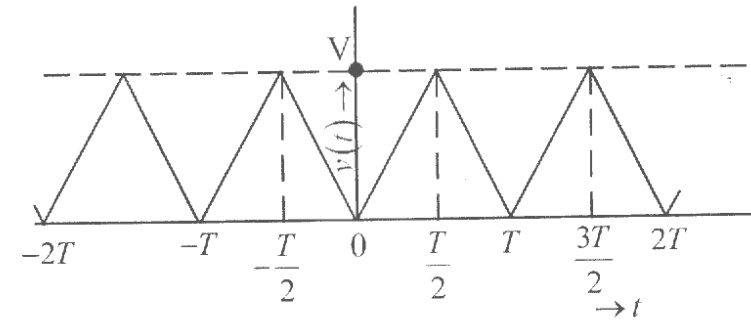


Fig. 8.

RGPVONLINE.COM

Unit - V

9. a) Discuss the restrictions on poles and zeros locations in s-plane for driving points locations.
- b) For the network shown in Fig. 9 determine the voltage-ratio transfer function, $\frac{V_2(s)}{V_1(s)}$

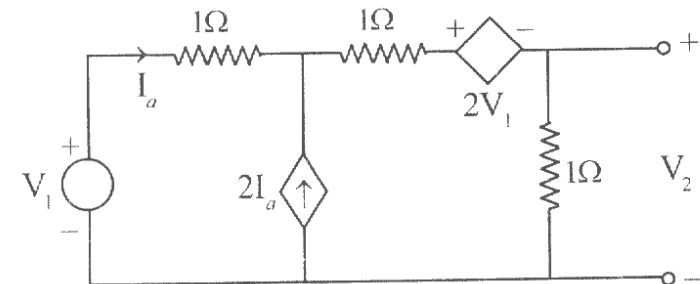


Fig. 9