

Total No. of Questions : 8]

[Total No. of Printed Pages : 4

Roll No

EC-222 (CBCS)**B.E. III Semester**

Examination, December 2017

Choice Based Credit System (CBCS)**Network Analysis****Time : Three Hours****Maximum Marks : 60**

- Note:** i) Attempt any five questions.
ii) All questions carry equal marks.

1. a) Calculate the voltage (V) in the circuit of Figure 1.

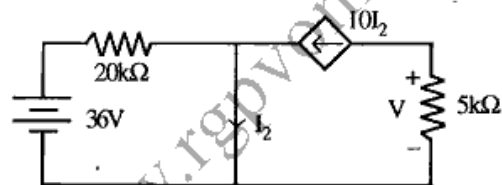


Figure 1

- b) Determine I in the circuit shown in Figure 2.

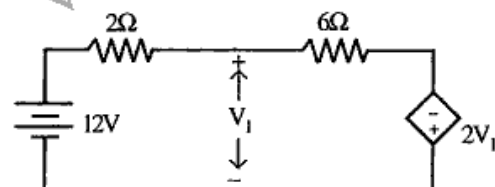


Figure 2

- c) Write the KCL equations for the circuit shown in Figure 3.

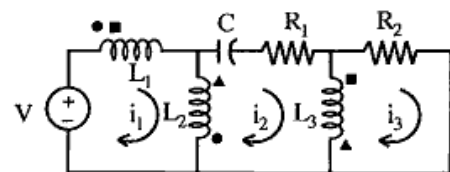


Figure 3

184

[2]

2. a) For the network shown in Figure 4, draw network graph. Obtain the basic cutsets and write basic cutset matrix.

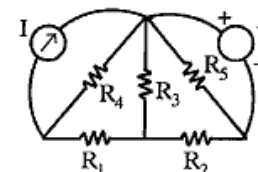


Figure 4

- b) For the network shown in Figure 5. Obtain the incidence matrix, the node admittance matrix and the matrix node equation.

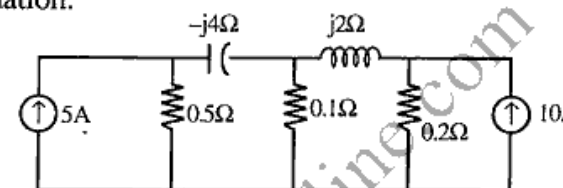


Figure 5

3. a) Find the Norton equivalent of the network shown in Figure 6.

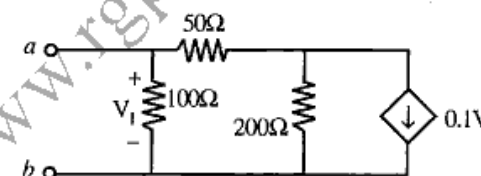


Figure 6

- b) Determine the value of R_L to be connected across AB in Figure 7, for maximum power transfer. Also calculate the maximum power absorbed by R_L .

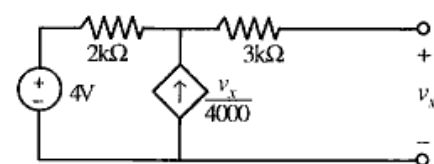


Figure 7

184

[3]

4. a) State and prove reciprocity, and compensation theorems.
b) State and prove Tellegen's theorem.

5. a) Find the current $i(t)$ for the network shown in Figure 8 if the voltage source $v(t) = 2e^{-0.5t} u(t)$ and $v_c(0^+) = 0$

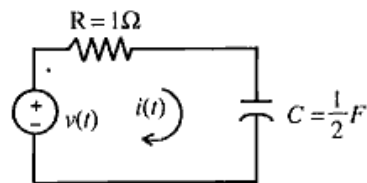


Figure 8

- b) At $t = 0$, s is closed in the circuit of figure 9, find $v_c(t)$ and $i_c(t)$. All initial conditions are zero

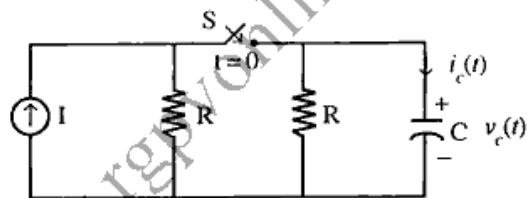


Figure 9

6. Calculate the current in 6Ω resistor of the circuit of Figure 10 by
i) Thevenin's theorem
ii) Superposition theorem

Use Laplace transform method:

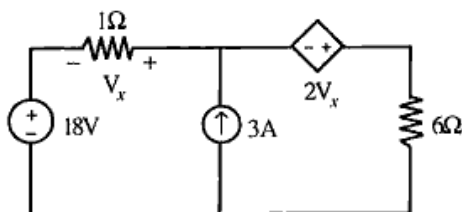


Figure 10

185

PTO

[4]

7. a) Determine the Z-parameters for the network shown in figure 11.

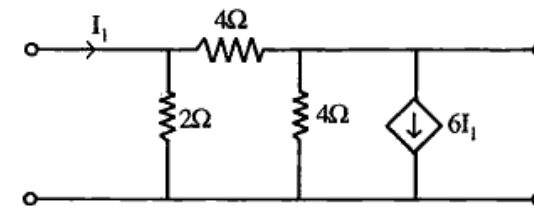


Figure 11

- b) Obtain the Z-parameters of the network shown in figure 12.

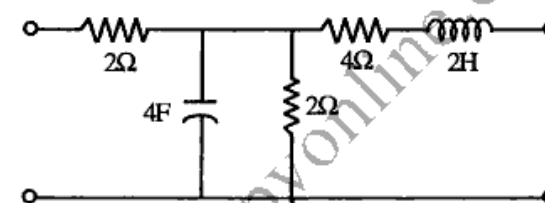


Figure 12

8. Write short notes on any two of the following:
a) Parallel resonance
b) Maximum power transfer theorem
c) Hybrid parameters

186