Total No. of Questions: 87

[Total No. of Printed Pages: 4

Roll No .....

**EX-602 (GS)** 

**B.E. VI Semester** 

Examination, May 2018

**Grading System (GS)** 

**Control Systems** 


Time: Three Hours

Maximum Marks: 70

Attempt any five questions out of eight. Note: i)

All questions carry equal marks.

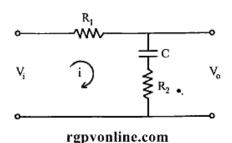- Describe the open-loop and closed-loop system. Also mention the advantages and disadvantages of open-loop and closed-loop control system.
  - Determine the transfer function of the following network.



rgpvonline.com

rgpvonline.com

rgpvonline.com


[2]

- Explain the following terms with reference to SFG (Signal Flow Graph):
  - Input node
  - Output node
  - iii) Chain node
  - iv) Forward path
  - Feedback loop/Feedback path
  - vi) Path gain

rgpvonline.com

rgpvonline.com

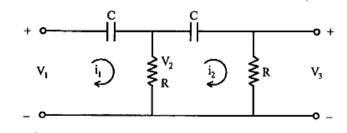- vii) Non-touching path
- Describe the construction and working of motor suitable for the use in a.c. servo system. Give the torque speed characteristics and derive the transfer function of it. 7
- Obtain signal flow graph and hence the transfer function of the circuit by Mason's gain formula.



What are the different types of Control action? Explain effect of each control action on system performance. 7

rgpvonline.com

rgpvonline.com

EX-602 (GS)

PTO

rgpvonline.com rgpvonline.com

rgpvonline.com

rgpvonline.com

Contd...

rgpvonline.com

EX-602 (GS)

7 each

[4]

[3]

Characteristic equation of a system is given as:

$$S^6 + 2S^5 + 8S^4 + 12S^3 + 20S^2 + 16S + 16 = 0$$

Find the roots to ascertain if it is marginally stable or unstable.

What are the difficulties arising in the Routh-Hurwitz stability criterion? How these difficulties are overcome?

Sketch the complete root locus of the system having:

$$G(s)H(s) = \frac{K}{s(s+1)(s+2)(s+3)}$$

Find the range of K, over which the system is stable.

Sketch the Bode plot of the transfer function: 14

$$G(s) = \frac{4}{s(1+s)(2+s)}$$

Determine the:

rgpvonline.com

rgpvonline.com

- Phase margin
- Gain margin

EV 60270381

- Describe the phase-lead compensation circuit and find out the transfer function.
  - What are the effects of Phase Lag compensation on the system performance?

Write a short note on any two of the following:

- Standard Test Signals
- Poles and Zeros
- Power amplifier

rgpvonline.com

rgpvonline.com

rgpvonline.com

-gpwonline.com

EX-602 (GS)

rgpvonline.com rgpvonline.com

rgpvonline.com

rgpvonline.com

 $\Omega$ TQ